

# MODULE 1



## Module - 1

# Semiconductor diodes and Applications

SYLLABUS: .....	1
TEXTBOOKS: .....	1
The pn junction – formation and working .....	1
Biased junction - Operation .....	3
pn-junction diode as a switch .....	6
Diode parameters .....	7
Types of Break down .....	9
Diode approximation - Equivalent circuit: .....	11
Rectifiers .....	15
Half-wave rectifier .....	15
Full wave rectifier - center-tapped – operation and waveforms .....	23
Full wave bridge rectifier – operation and waveform .....	28
Comparison of rectifiers .....	33
Capacitor filter circuit .....	34
Zener diode voltage regulator .....	36
Photodiode .....	40
Light Emitting Diode (LED) .....	41
Photo Coupler .....	42
LM 78XX series Voltage Regulator .....	43
QUESTION BANK .....	44

### SYLLABUS:

*p-n junction diode, Equivalent circuit of diode,  
Zener Diode, Zener diode as a voltage regulator,  
Rectification-Half wave, Full wave – Bridge & centre tapped rectifier,  
Capacitor filter circuit (2.2, 2.3, 2.4 T1).  
Photodiode, LED, Photocoupler (2.7.4, 2.7.5, 2.7.6 T1)  
78XX series and 7805 Fixed IC voltage regulator (8.4.4 and 8.4.5 of T1)*

### TEXTBOOKS:

*T1. "Basic Electronics", D.P. Kothari, I. J. Nagrath, McGraw Hill Pvt Ltd, 2014.  
T2. "Electronic Devices", Thomas L Floyd, Pearson Education, 9<sup>th</sup> edition 2012*

### The pn junction – formation and working


This shall be studied under three headings as given below .

#### FORMATION:

1. A pn junction is formed by joining a **p-type** and **n-type** semiconductor. The holes are the majority charge carriers in **p-type** and electrons in the **n-type** semiconductor.
2. The majority charge carriers are **uniformly distributed in the semiconductor**.
3. Majority holes from P side diffuse into N side and vice versa as shown in Fig.1.1.

#### JUNCTION FORMATION AND MOVEMENT

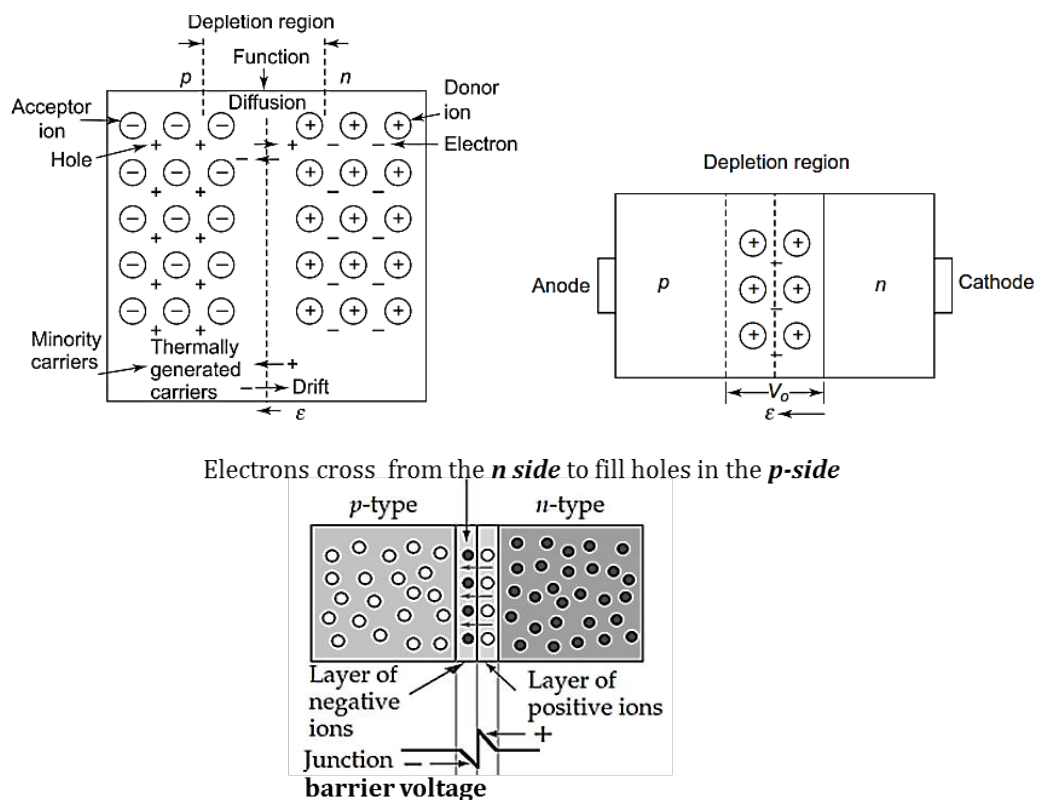1. The movement of majority charge carriers across the junction is called as **DIFFUSION** from a region of high carrier concentration to a region of low carrier concentration.
2. When the -ve ions are created on the **p-type** due to diffusion, the portion close to the junction on **p-type** acquires a -ve voltage. Similarly when the +ve ions are created on the n-type, the portion close to the junction on **n-type** acquires a +ve voltage.
3. The negative voltage on **p-type** repels additional electrons crossing the junction and the +ve voltage on **n-type** repels the additional holes crossing the junction.
4. The electric field set up by the +ve and -ve ions by diffusion of charge carriers prevents further flow of electrons and holes creating a potential difference at the junction known as **BARRIER VOLTAGE**.
5. The **magnitude of barrier voltage depends on doping densities, electronic charge and junction temperature**.
6. The barrier voltage opposes the flow of majority carriers across the junction but assists the flow of minority carriers across the junction in in opposite direction, known as a **DRIFT CURRENT**.



7. Fig.1.1: pn junction

## DEPLETION REGION

1. A region is known as **DEPLETION REGION** *that is depleted of charge carriers is formed because of the movement of majority charge carriers across the junction that leaves a layer on each side where no charge carriers/free electrons and holes are present..*
2. On *n-type* the depletion region consists of donor impurity and on *p-type* the depletion region consists of acceptor impurity.
3. If the semiconductors have equal doping densities, then the depletion layers on each side have same widths.
4. It is to be noted that, In steady-state, there is no net current flow across the junction.

### Summary - p-n junction

1. The majority holes from P-side **diffuse** into N-side and vice versa.
2. Recombination of electrons and holes in a narrow region on both sides of the junction results in uncovered fixed positive ions on N-side and fixed negative ions on P-side. This is the **depletion region** where no free electrons and holes are present.
3. The electric field set up by the positive and negative ions prevents further flow of electrons and holes – called **Barrier Potential**.
4. The electric field causes the movement of minority carriers in opposite direction, a **drift current**.
5. In steady-state, there is no net current flow across the junction.

### Biased junction - Operation

When an external voltage is applied to a pn junction, the pn junction is said to be biased.

#### Forward-biased junction

1. When the **positive terminal is connected to p-type** and negative terminal to **n-type**, the electrons from the **n-type** are repelled from the -ve terminal and holes from the **p-type** are repelled from the +ve terminal as shown in Fig.1.2.
2. *This reduces the width of the depletion region and the barrier potential.*
3. When the *applied bias voltage increases the barrier voltage decreases* and it disappears. *The majority charge carriers can easily flow across the junction.*

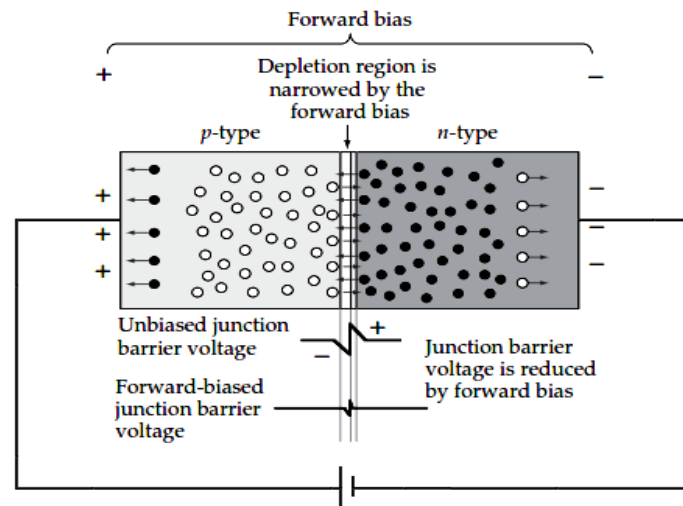


Fig.1.2: pn junction under forward bias

4. A majority charge carrier current flows and the junction is said to be forward biased.
5. *Increase in the bias voltage further from zero after the **knee** of the characteristics the barrier potential is overcome and allows more majority charge carriers to flow across the junction, causing a very large current for very small increments in input voltage.*

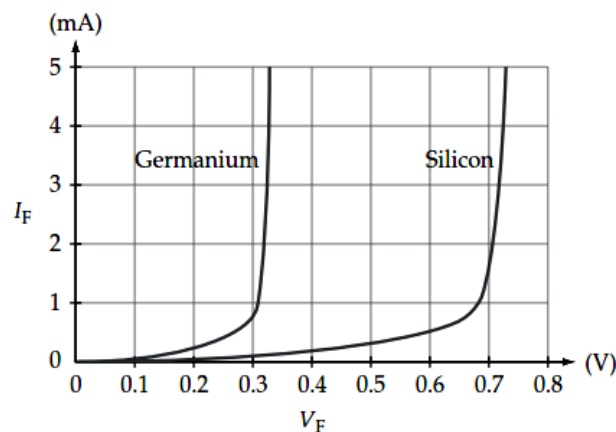


Fig.1.3: Forward -bias characteristics Si and Ge

### Reverse-biased junction

1. When **positive terminal connected to *n-type*** and **negative terminal to *p-type***, the electrons from ***n-type*** are attracted to the +ve terminal and holes from the ***p-type*** are attracted to the -ve terminal as shown in Fig.1.4.
2. **This widens the depletion region and the barrier voltage increases.**
3. When barrier voltage increases there is no possibilities of majority carrier current flow across the junction and the **junction is said to be reverse biased and has a high resistance.**

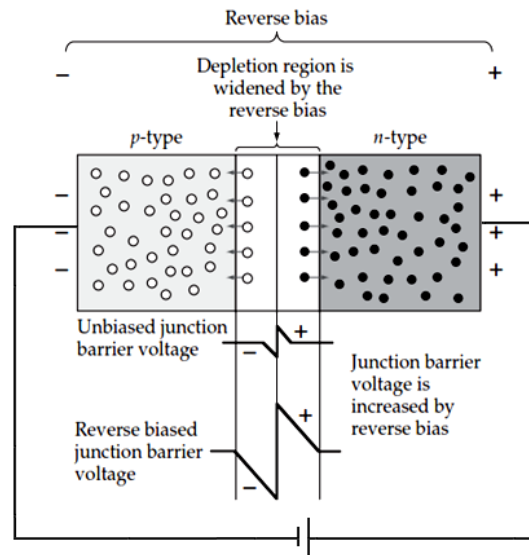


Fig.1.4: pn junction under Reverse bias

- The *minority carriers on each side can still cross the junction or DRIFT* and their movements across the junction results in a **small reverse current but stays at the saturation level**.
- Increase in the bias voltage further does not increase the current** level and this current is known as **REVERSE SATURATION CURRENT due to DRIFT**, which is almost of negligible order (nA for Si and uA for Ge).

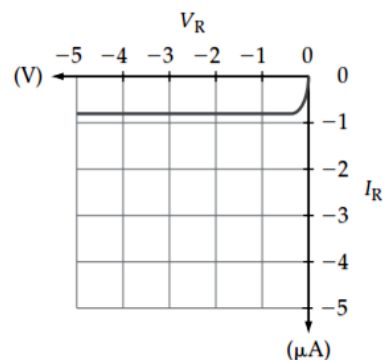


Fig.1.5: Reverse bias junction and characteristics

### Summary - biasing of a p-n junction

- A p-n junction is forward biased when **p is connected to the +ve and n to the -ve** terminal of the supply (**P-P N-N**). The **majority charge carriers current** is established **in a forward-biased** p-n junction.
- The **depletion layer width narrows down** on application of **forward voltage**.
- Barrier potential for Germanium is 0.3 V and for silicon is 0.7 V at room temperature. These are the voltage drops across the p-n junction when current flows.
- When **p-connected to the -ve and n connected to the +ve** terminal of the supply, the p-n junction is said to be **reverse biased (P-N N-P)**. A minutely **small**

**current flows** through a **reverse-biased** p-n junction due to the **minority charge carriers**.

5. The **width of the depletion layer, & the barrier potential increases** when the **junction is reverse biased**.
6. A **forward-biased** p-n junction offers **ALMOST NO resistance** to current flow while a **reverse-biased** junction offers **VERY HIGH resistance**.

## LINKS TO VIDEOS

**Introduction to Semiconductors** <https://www.youtube.com/watch?v=qAbqWwKcUAE>

**p-n junction diode forward and reverse biased** <https://www.youtube.com/watch?v=Coy-WRCfems>


<https://www.youtube.com/watch?v=USrYQJspDEg>

**Introduction to Diode: V-I characteristics of the Diode:**

<https://www.youtube.com/watch?v=EdUAecpYVWQ>

## pn-junction diode as a switch

1. A junction can be used as a switch, i.e. ON when forward biased and **OFF** when reverse biased.
2. A pn-junction provided with copper wire connecting leads becomes an electronic device known as diode.
3. The circuit symbol for a diode is an *arrowhead and a bar*. The **arrowhead indicates the direction of current flow when the diode is forward bias** as shown in the Fig.1.6.
4. The **p-type** of the diode is always the +ve terminal for forward bias and is termed as anode. The **n-type** of the diode is always the -ve terminal for forward bias and is termed as cathode.

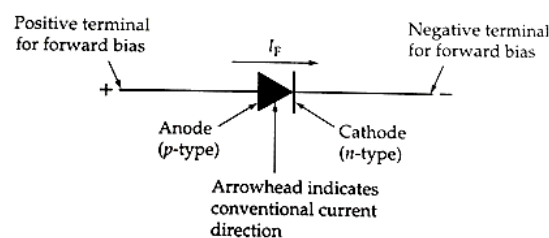

**Fig.1.6: pn-junction diode**

## Diode relationship and VI characteristics

$$I_D = I_0 \left( e^{\frac{(kV_D)}{T_k}} - 1 \right)$$

where  $I_0$  is the reverse saturation current

$k = 11,600/\eta$  Boltzman's constant  $\eta=1$  for Ge and  $\eta=2$  for Si for low current, below the knee of the curve and  $\eta=1$  for both Ge and Si for higher level of current beyond the knee

$T_k = T_c + 273^\circ$ , and

$T_c$  = operating temperature ( $25^\circ\text{C}$ )

The plots of Eq. (14.1) for Ge and Si diodes are drawn to scale in Fig. 14.5. The sharply rising part of the curve extended downward meets the  $V_D$  axis, which is indicated

$V_\gamma = V$  suffix **Gamma** - offset, threshold or firing potential

One may assume  $I_D = 0$  up to  $V_T$  and then increases almost linearly at a sharp slope. The values of  $V_T$  are

$V_\gamma = 0.7V$  for Si diode

$V_\gamma = 0.3V$  for Ge diode

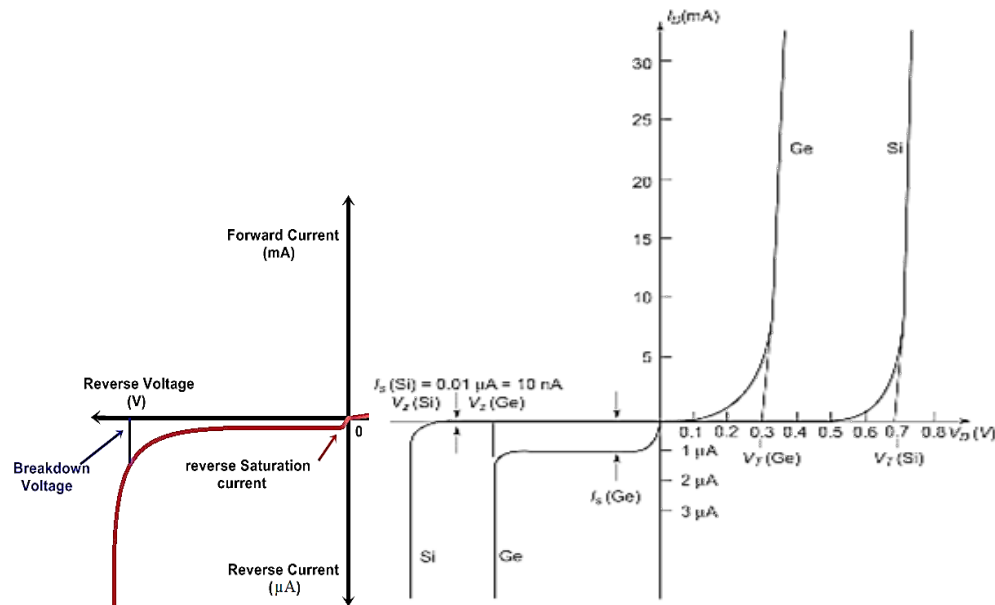


Fig.1.7: Si and Ge - pn junction diode characteristics

## Problem

An Si diode has  $I_S = 10 \text{ nA}$  operating at  $25^\circ\text{C}$ . Calculate  $I_D$  for a forward bias of  $0.6 \text{ V}$ .

**Solution** We take  $\eta = 2$

$$T_k = 25^\circ + 273^\circ = 298^\circ$$

$$k = \frac{11,600}{2} = 5,800$$

$$kV_D/T_k = \frac{5800 \times 0.6}{298} = 11.68$$

$$e^{11.68} = 117930$$

$$\text{Then } I_D = 10 (117930 - 1) = 50 \times 0.117929 \times 10^6 \text{ nA} \\ = 0.586 \text{ mA, negligible.}$$

This justifies the choice of  $\eta = 2$

**Note:** The diode is to conduct current much larger than this value.

So  $I_D = 0.586 \text{ mA}$  may be approximated as zero.

## Diode parameters

The diode parameters required for the construction of diode characteristics are

- i. Forward voltage drop ( $V_F$ )
- ii. Maximum forward current ( $I_{F(\max)}$ )
- iii. Reverse breakdown voltage ( $V_{BR}$ )
- i. Reverse saturation current ( $I_o$ )
- ii. Dynamic resistance ( $r_d$ )



**Knee Voltage / Forward Voltage ( $V_F$  also):** Forward voltage drop at a given temperature is defined as the maximum forward voltage of the diode for a specific forward current, it is also given by the relation,

$$\text{Forward Voltage Drop} = \frac{\text{Power Dissipated}}{\text{Forward DC Current}} = \frac{P_D}{I_F}$$

**Maximum Forward Current ( $I_{Fmax}$ ):** Every diode has a maximum value of forward current that may be passed continuously through the diode safely is known as maximum forward current, if this value is exceeded, then the diode is destroyed due to excessive heat.

**Reverse Saturation Current ( $I_0$ ):** It is the maximum reverse current that flows through a reverse biased P-N junction at a given temperature, this current is only due to MINORITY CARRIERS, by DRIFT action its value is  $<1\mu\text{A}$  for silicon and around  $100\mu\text{A}$  for germanium diodes.

**Reverse Breakdown Voltage ( $V_{BR}$ ):** It is the maximum reverse voltage applied at which the P-N junction breaks down and reverse current rises sharply. This critical value of voltage is known as **breakdown voltage**. Breakdown voltage is around 50V for Germanium diode and 75V for Silicon diode.

**Power Dissipation ( $P_D$ ):** The power dissipated in a diode for a given value of diode voltage ( $V_D$ ) and current ( $I_D$ )

$$P_D = I_D * V_D$$

**Static Resistance / DC Resistance ( $R_{DC}$ ):** It is the opposition offered by the P-N junction to the flow of DC current when in forward bias, it is measured by taking a ratio of DC voltage across diode to the resulting DC current through it. It is given by,  $R_{DC} = \frac{V_F}{I_F}$   $R_{DC}$  varies from  $40\Omega$  to  $70\Omega$ .

1. Calculate the forward and reverse resistances offered by a silicon diode with  $I_F = 100\text{mA}$ ,  $V_F = 0.75\text{V}$  and  $V_R = 50\text{V}$ ,  $I_R = 1\mu\text{A}$ .

$$\text{Forward resistance is given by : } R_F = \frac{V_F}{I_F} = \frac{0.75}{100\text{m}} = 7.5\Omega$$

$$\text{Reverse resistance is given by : } R_R = \frac{V_R}{I_R} = \frac{50}{1\mu} = 500\text{M}\Omega$$

**Dynamic Resistance ( $r_d$ ):** Dynamic resistance also called incremental resistance for a diode at a given temperature is the reciprocal of the slope of the forward characteristics, given by  $r_d = \left. \frac{\Delta V_F}{\Delta I_F} \right|_{\text{at a given temperature maintained constant, or from the diode VI characteristics}}$

$\Delta V_F$  is the change in the forward voltage and  $\Delta I_F$  is the change in the forward current.

Also for any temperature T at which the junction is maintained,

$$r_{d \text{ at } T} = \frac{26\text{mV}}{I_F} \left( \frac{T + 273^\circ\text{C}}{298^\circ\text{C}} \right) \Bigg|_{\text{for Si}}$$

Volt equivalent for Si = 26mV  
at room temperature  
 $r_d$  is often very small – few ohms

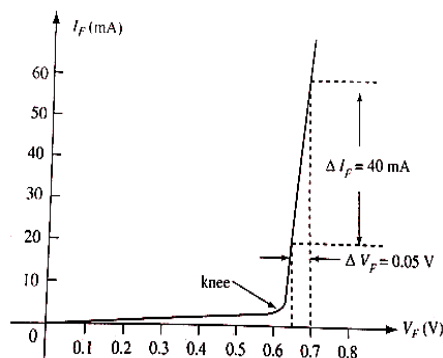


Fig.1.8: pn junction diode characteristics

**Peak inverse voltage:** It is the maximum voltage that a diode can withstand in the reverse direction without breaking down. If this voltage is exceeded the diode may be destroyed. Diodes must have a peak inverse voltage rating that is higher than the maximum voltage that will be applied to them in a given application.


**Maximum power rating:** It is defined as the maximum power that a diode can dissipate without damaging it is called maximum power rating. Usually, maximum power rating is specified by the manufacturer in its data sheet. The power dissipated at the junction is equal to the product of junction current and the voltage across the junction. If the power developed across the junction is more than the maximum power dissipated by it, the junction will be over-heated and may be destroyed.

#### LINKS TO VIDEOS

*Diode Resistance Explained (DC, AC and Average AC Resistance):*

<https://www.youtube.com/watch?v=hag5ss1ZxH0>

### Types of Break down

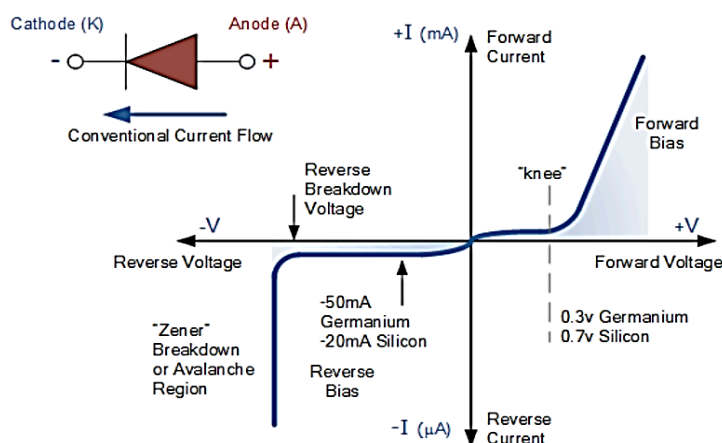

**Zener Region** As the reverse-bias voltage is raised, the diode breaks down at voltage  $V_v$  by **AVALANCHE PHENOMENON**.

- The maximum negative voltage that a diode can withstand at Peak Inverse Voltage (PIV rating). The avalanche breakdown occurs when a **very high reverse voltage** is applied across the diode.
- As the applied reverse voltage increases, the electric field across the junction increases, it exerts a **FORCE ON THE ELECTRONS AT THE JUNCTION AND FREES THEM FROM COVALENT BONDS**. These free electrons start moving with

high velocity across the junction and collide with the other atoms, thus creating more free electrons.

- This results in the rapid increase in net current. Both kinds of breakdowns occur in Zener diodes. The avalanche breakdown occurs because of the ionisation of electrons and hole pairs whereas the Zener breakdown in zener diode occurs because of heavy doping.

**Zener Breakdown** **HEAVY DOPING** of the N and P-regions can result in **low breakdown voltage** of just a few volts —10 V, —5 V. This mechanism of breakdown is different from avalanche and the type of diode called **zener** diode.

- When connected at a point in an electronic circuit, it does not allow the potential there to exceed the diode rated voltage.
- When the diode is reverse biased, the **KINETIC ENERGY OF THE ELECTRONS INCREASES** and they move at higher velocities colliding with other atoms giving rise to free electrons.
- These free electrons, in turn, give rise to a very high value of reverse saturation current. This is Zener breakdown.

#### COMPARISON TABLE OF AVLANCHE ND ZENER BREAKDOWN


Avalanche Breakdown	Zener Breakdown
1. The process of applying <b>high voltage and increasing the free electrons</b> or electric current in semiconductors and insulating materials, by breaking <b>COVALENT BONDS</b>	The process in which the <b>electrons move across the barrier</b> from the valence band of p-type material to the conduction band of n-type material
2. Breakdown voltages much greater than 10 volts.	Zener breakdown voltage of 5 to 8 volts.
3. The valence electrons are pushed to conduction due to the energy imparted <b>by accelerated electrons</b> , which gain their velocity due to their collision with other atoms.	The valence electrons are pulled into conduction due to the high electric field <b>in the narrow depletion region</b> .
4. The increase in temperature <b>increases</b> the breakdown voltage.	The increase in temperature <b>decreases</b> the breakdown voltage.
5. The VI characteristic curve of the avalanche breakdown is not as sharp as the Zener breakdown.	The VI characteristics of a Zener breakdown has a sharp curve.
6. DEPLETION REGION : THICK - It occurs in diodes that are lightly doped.	THIN DEPLETION REGION Because It occurs in diodes that are <b>highly doped</b> .
7. Junction destroyed after breakdown as thr	Junction isn't destroyed, rather re used many times after breakdown
8. Positive temperature coefficient – breakdown voltage increases with temperature	-ve temperature coefficient – breakdown voltage decreases with temperature
9. Ionization occurs because of collision	Ionization occurs because of electric field

## LINKS TO VIDEOS

**Avalanche Breakdown and Zener Breakdown Effect (detailed) :** <https://www.youtube.com/watch?v=EzL5qjiMltc>

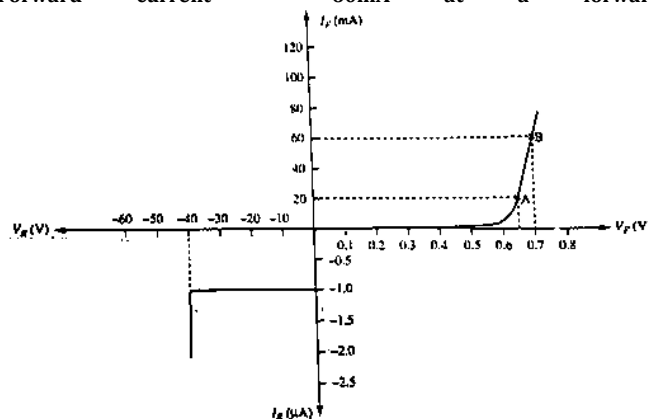1. Plot the forward and reverse characteristics of a diode for the following data

- Forward voltage drop = 0.6V
- Reverse breakdown voltage = 40V
- Reverse saturation current = 1  $\mu$ A
- Forward current = 20mA at a forward voltage of 0.65V
- Forward current = 60mA at a forward voltage of 0.7V



Determine the dynamic resistance at a forward current of 40mA for the diode characteristics given in the Fig.1.8

$$r_d = \frac{\Delta V_F}{\Delta I_F} = \frac{0.05}{40\text{m}} = 1.25\Omega$$

### Diode approximation - Equivalent circuit:

- Equivalent circuit of a device is a proper *combination of electrical elements like voltage source, current source, resistor etc to represent* the actual terminal characteristics.
- Diodes are one way devices, offering a low resistance when forward biased and a high resistance when reverse biased. Equivalent circuit for a diode can be obtained by approximating the VI characteristics by straight line segments.
- There are **3 types of equivalent circuits or approximations**

#### 1. Ideal diode approximation

- Diodes are one way devices, offering a low resistance when forward biased and a high resistance when reverse biased.
- An **ideal diode** (or perfect diode) would have **zero forward resistance** and zero forward voltage drop. It would also have an **infinitely high reverse resistance**, which would result in zero reverse current.

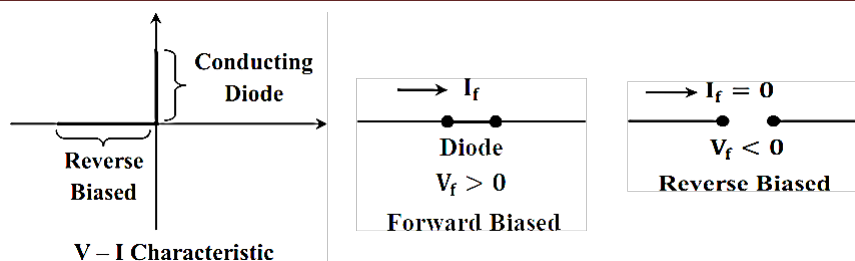


Fig.1.9: Ideal diode approximation: characteristics and equivalent circuit

## 2. Practical diode approximation

- Although an ideal diode does not exist, diodes can be assumed to be near-ideal devices with forward voltage drop and are called as **practical diodes**.
- For **silicon diode the forward drop is 0.7V** and **Germanium - forward drop is 0.3V**

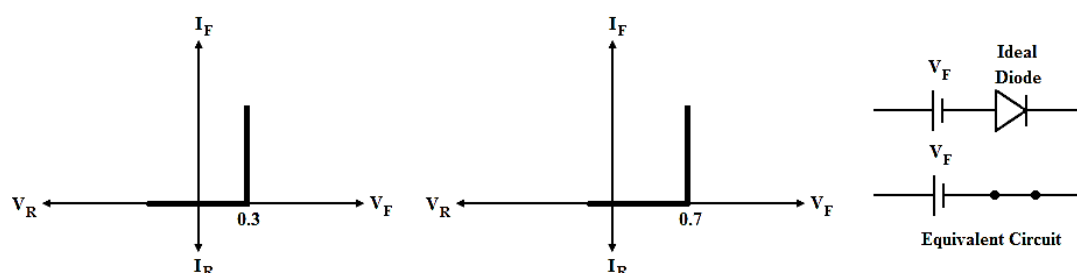


Fig.1.10: Practical diode approximation: characteristics and equivalent circuit

## 3 Piecewise Linear approximation

- When a forward characteristics of a diode is not available a straight line approximation called piecewise linear characteristics can be used.
- In a forward bias, diode is assumed to have a constant forward voltage drop ( $V_F$ ) and negligible series resistance (dynamic resistance).
- To construct a piecewise linear characteristics,  $V_F$  is marked first on the horizontal axis (point X). Then from  $V_F$  a straight line is drawn with a **slope**

**equal to  $(1/r_d)$   $r_d$  - the diode dynamic resistance**

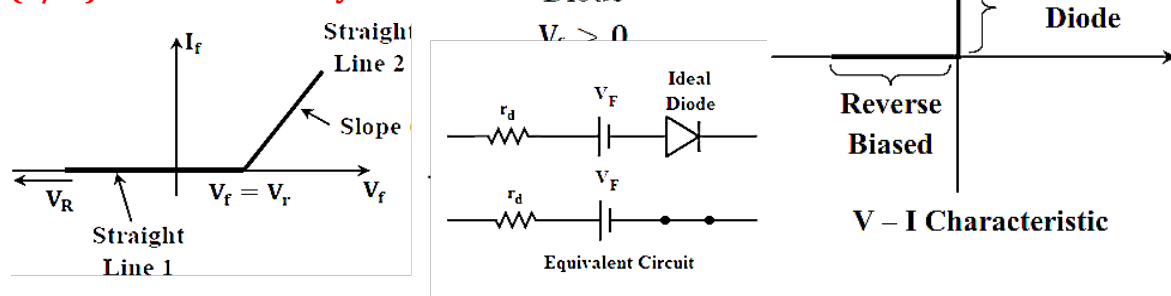



Fig.1.11: Piecewise linear approximation: characteristics and equivalent circuit

## LINKS TO VIDEOS

*Ideal Vs Practical Diode* : <https://www.youtube.com/watch?v=WX0xQWRTpj8>
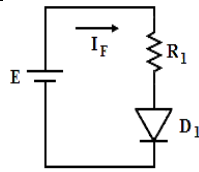
## Problems:

- Calculate the diode current for the given circuit having a silicon diode with a resistance of  $4.7k\Omega$  and  $E = 15V$



Applying KVL to the circuit we get :  $E = I_F R_1 + V_F$  ( $V_F$  = voltage drop across diode)

The diode current is taken on one side to get  $I_F = \frac{E - V_F}{R_1} = \frac{15 - 0.7}{4.7K}$

$$I_F = 3.04\text{mA}$$

2. Calculate the diode current for the circuit given before having a silicon diode with a resistance of  $1k\Omega$  and  $E = 12V$

Apply KVL on the circuit we get  $E = I_F R_1 + V_F$


The diode current is got as  $I_F = \frac{E - V_F}{R_1}$   $I_F = \frac{12 - 0.7}{1K}$

$$I_F = 11.3\text{mA}$$

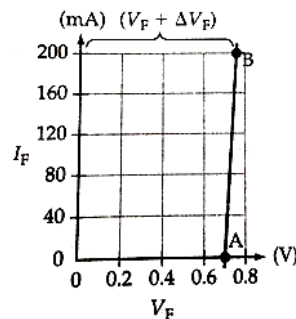
3. Construct a piecewise linear characteristics for a silicon diode which has a  $0.25\Omega$  dynamic resistance and a  $200\text{mA}$  maximum forward current.

$r_d = \frac{\Delta V_F}{\Delta I_F}$  re arranging we get  $\Delta V_F = r_d * \Delta I_F$  Hence -  $\Delta V_F = 200\text{m} * 0.25 = 0.05V$


- To draw the piecewise linear characteristics mark point A at  $V_F = 0.7V$  on the horizontal axis
- At  $200\text{mA}$  mark point B at  $V_F = 0.7V + 0.05V = 0.75V$  on the horizontal axis
- The piecewise linear characteristics for the given problem is as shown in the Figure below.



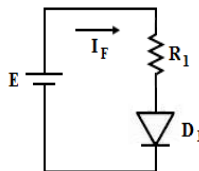4. Calculate  $I_F$  for the diode in the given circuit assuming that  $V_F = 0.7V$ ,  $E = 1.5V$ ,  $R_1 = 10\Omega$  and  $r_d = 0$ . What is the current if we consider  $r_d = 0.25\Omega$



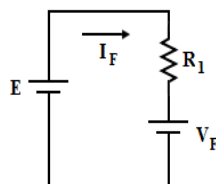
- Equivalent circuit of the diode when dynamic resistance is neglected is obtained by replacing diode with a voltage cell with a voltage  $V_F = 0.7V$



- Applying KVL on the equivalent circuit when  $r_d = 0$  we get

$$E = I_F R_1 + V_F \text{ re arranging - } I_F = \frac{E - V_F}{R_1} = \frac{1.5 - 0.7}{10} = 80\text{mA}$$

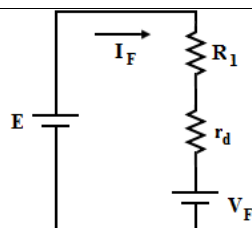- Equivalent circuit of the diode with a dynamic resistance is obtained by replacing diode with a voltage cell with a voltage  $V_F = 0.7V$  and dynamic resistance  $r_d$ .




- Applying KVL on the equivalent circuit when  $r_d = 0.25\Omega$  we get

$$E = I_F R_1 + I_F r_d + V_F$$


$$I_F = \frac{E - V_F}{R_1 + r_d} = \frac{1.5 - 0.7}{10 + 0.25} = 78\text{mA}$$

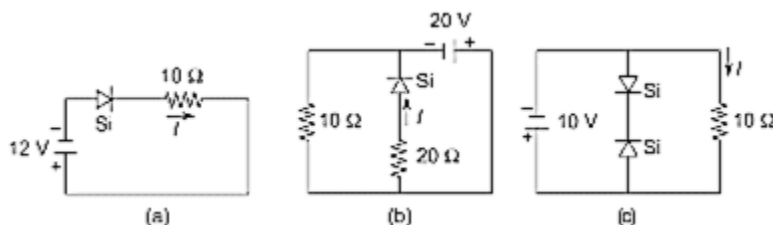**5. For the diode in the circuits given below, find I**




- Reverse biased by 12 V hence doesn't conduct  $I=0$
- Voltage across the diode here is 20V independent of 10 ohm res. Diode conducts as per the equivalent circuit, we have  $I = \frac{20-0.7}{20} = 0.965\text{A}$
- Both diodes are in opposition hence no current flows in left loop,  $I = \frac{10}{10} = -1\text{A}$

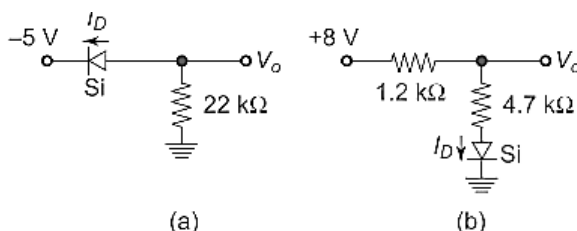**6. For the following ckts determine  $I_D$  and  $V_o$  using the approximate model**



- Redrawing we get

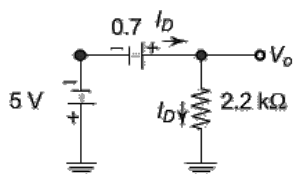


$$I_D = \frac{5 - 0.7}{2.2} = \frac{4.3}{2.2} = 1.95\text{mA}$$

$$V_o = 2.2 I_D = 2.2 \times \frac{4.3}{2.2} = 4.3\text{V}$$

or directly,

$$V_o = 5 - 0.7 = 4.3\text{V}$$


- Redrawing :

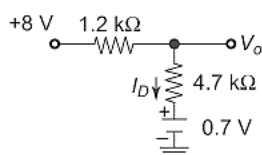

$$I_D = \frac{8 - 0.7}{1.2 + 4.7} = \frac{7.3}{5.9} = 1.237\text{mA}$$

$$V_o = 4.7 \times 1.237 + 0.7 = 6.51\text{V}$$

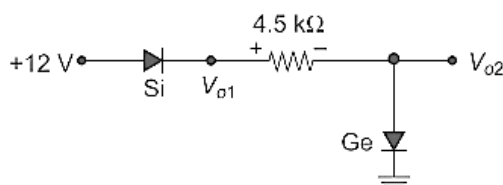**7. For the network determine  $V_{o1}$  &  $V_{o2}$  using the approximate model**




$$V_{o2} = 0.3 \text{ V or } V_T(\text{Ge}) = 0.3 \text{ V when conducting}$$

$$V_{o1} = 12 - 0.7 = 11.3 \text{ V}$$

Note the result does not depend on  $4.5 \text{ k}\Omega$ .
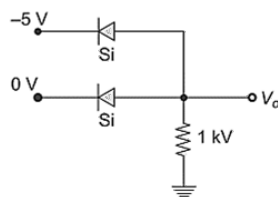
### 8. Determine $V_o$ for the negative logic OR gate



For given input voltages we see that

$$\text{only top diode conducts } V_o = -5 + 0.7 = -4.3 \text{ V}$$

Now we give -5V to any or both inputs we get an output of -4.3 V (HIGH)

Output becomes Zero if no inputs are given 0 volts

Rev biased lower diode remains OFF

### LINKS TO VIDEOS

**PROBLEM: HOW TO SOLVE THE DIODE CIRCUITS:** <https://www.youtube.com/watch?v=jkEVGQ2Inel>

**Diode Equivalent Circuits:** <https://www.youtube.com/watch?v=06Or9jeeZPM>

**PROBLEM: SERIES DIODE CONFIGURATION :** <https://www.youtube.com/watch?v=rl9FdHTVOWY>

**PROBLEM: PARALLEL AND SERIES-PARALLEL CONFIGURATION OF DIODES :**

<https://www.youtube.com/watch?v=4D0it39f2lQ>

## Rectifiers

- A rectifier is an electrical device that **converts an Alternating Current (AC) into a Direct Current (DC) by using one or more P-N junction diodes.**
- The rectifiers are mainly classified into two types:
  - Half wave rectifier
  - Full wave rectifier
- Half wave rectifiers use one diode, while a full wave rectifier uses multiple diodes.

### Half-wave rectifier

- Half-wave rectifiers allow only **one half-cycle (+ve half-cycle)** of the AC voltage through it and will block the other half-cycle (-ve half-cycle) of the AC voltage as shown in the Fig.1.12.

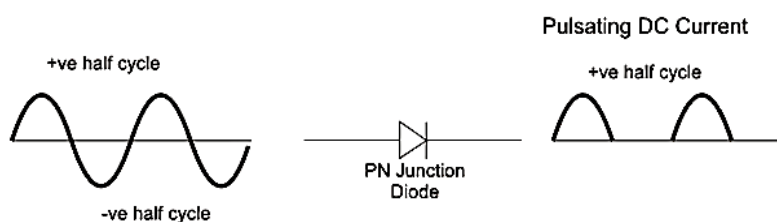


Fig.1.12: Half wave rectifier operation

### Operation of a half wave rectifier

- Fig.1.13 shows the circuit diagram of a rectifier using a step down transformer.



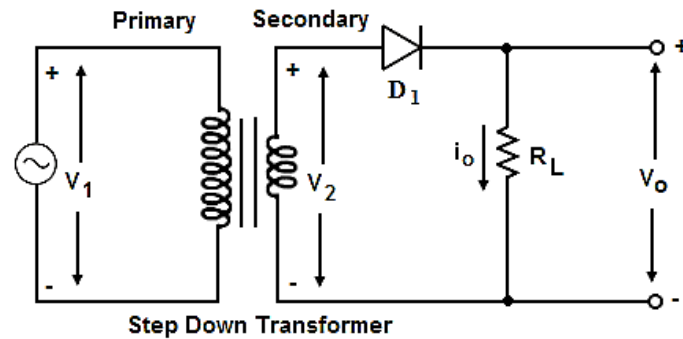


Fig.1.13: Half-wave rectifier

- The step down transformer reduces the AC supply voltage to the required level.
- The AC voltage to be rectified is applied across the primary of the transformer and the voltage across the secondary of the transformer is available for rectification.
- Half-wave rectifier rectifies only one half cycle of the AC input.
- Let the voltage applied across the primary of the transformer be  $v_1 = V_m \sin \omega t$  where  $V_m$  is the peak value
- The voltage across the secondary of the transformer available for rectification is given by


$$v_2 = \frac{N_2}{N_1} V_m \sin \omega t \quad \text{where } \frac{N_2}{N_1} \text{ is the turns ratio of the transformer}$$

$N_1$ : number of turns in the primary coil

$N_2$ : number of turns in the secondary coil

- If  $N_2 = N_1$   $v_2 = V_m \sin \omega t$


### Half wave rectifier waveforms

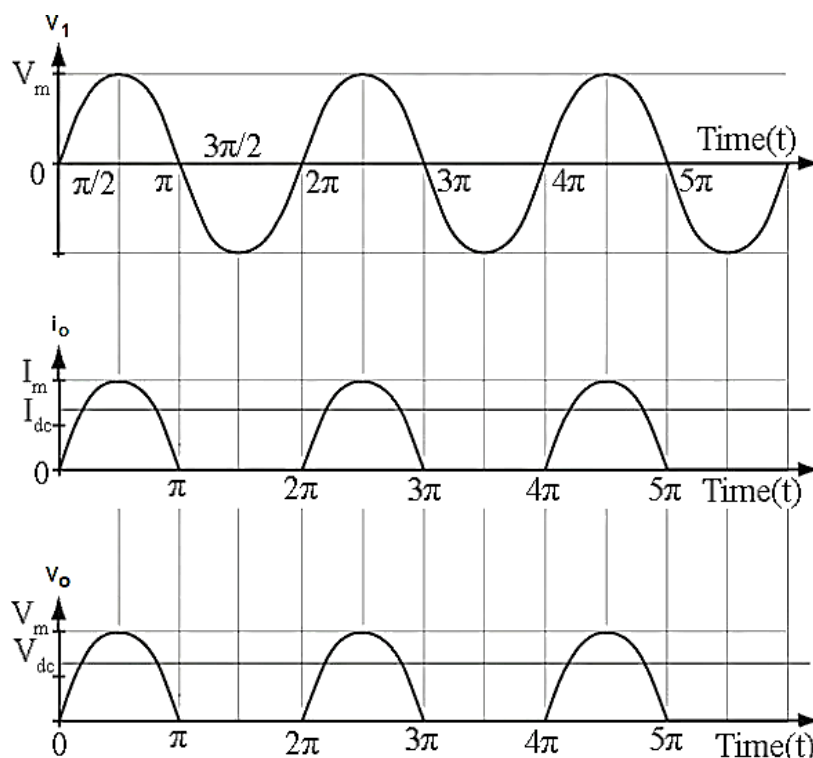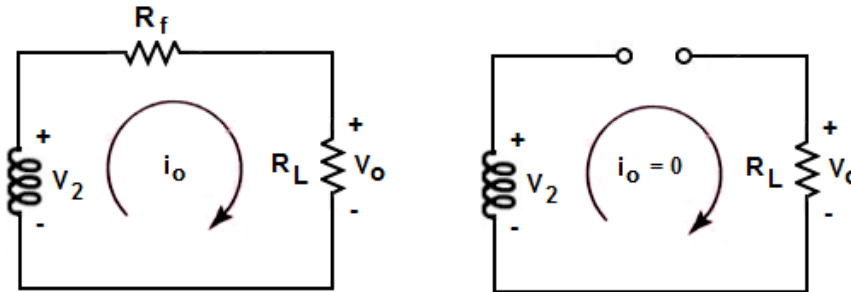

**Fig.1.14: Half-wave rectifier waveform**

- During the +ve half cycle the diode conducts and the current  $i_o$  flows through the load. The load voltage  $v_o = i_o R_L$ .
- During the -ve half cycle the diode gets reverse biased and the current  $i_o$  is zero. The load voltage  $v_o = 0$ .

**Hence during a total cycle the output waveform has only 1 +ve sinusoidal waveform corresponding to the time when the diode turns ON**

**Fig.1.15: Equivalent circuit to find half-wave rectifier current**

- From the circuit shown in the Fig.1.15  $i_o = \frac{v_2}{R_f + R_L}$

$$i_o = \frac{V_m \sin \omega t}{R_f + R_L}$$

$$i_o = I_m \sin \omega t$$

Where  $I_m = \frac{V_m}{R_f + R_L}$  is the peak load current

### Average DC load current

$$I_{DC} = \frac{\text{Area under one cycle of } i_o}{\text{Period of } i_o}$$

$$I_{DC} = \int_0^{2\pi} i_o d\omega t / 2\pi = \int_0^{2\pi} \frac{I_m \sin \omega t d\omega t}{2\pi}$$

$$I_{DC} = \frac{1}{2\pi} \left[ \int_0^{\pi} I_m \sin \omega t d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right]$$

$$I_{DC} = \frac{I_m}{2\pi} [-\cos \omega t]_0^{\pi}$$

$$I_{dc} = \frac{I_m}{\pi}$$

### Average DC load voltage

$$V_{DC} = I_{DC} R_L$$

$$V_{DC} = \left( \frac{I_m}{\pi} \right) R_L = \frac{1}{\pi} \left( \frac{V_m}{R_f + R_L} \right) R_L$$

$$V_{DC} = \frac{V_m}{\pi} \left( \frac{R_L}{R_f + R_L} \right) = \left( \frac{V_m/\pi}{\frac{R_f + R_L}{R_L}} \right)$$

$$V_{dc} = \left( \frac{V_m/\pi}{1 + \frac{R_f}{R_L}} \right)$$

### RMS load current

$$I_{RMS} = \sqrt{\frac{\text{Area under one cycle of } i_o^2}{\text{Period of } i_o}}$$

$$I_{RMS} = \sqrt{\int_0^{2\pi} \frac{i_o^2 d\omega t}{2\pi}} = \sqrt{\frac{1}{2\pi} \left[ \int_0^\pi I_m^2 \sin^2 \omega t d\omega t + \int_\pi^{2\pi} 0 d\omega t \right]}$$

$$I_{RMS} = I_m \sqrt{\frac{1}{2\pi} \int_0^\pi \frac{1}{2} (1 - \cos 2\omega t) d\omega t + 0} = I_m \sqrt{\frac{1}{4\pi} \left[ \int_0^\pi d\omega t - \int_0^\pi \cos 2\omega t d\omega t \right]}$$

$$I_{RMS} = \frac{I_m}{2} \sqrt{\frac{1}{\pi} \left[ (\omega t)_0^\pi - \left( \frac{\sin 2\omega t}{2} \right)_0^\pi \right]} = \frac{I_m}{2} \sqrt{\frac{1}{\pi} \left[ (\pi - 0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]}$$

$$I_{rms} = \frac{I_m}{2}$$

### RMS load voltage

$$V_{RMS} = I_{RMS} R_L$$

$$V_{RMS} = \left( \frac{I_m}{2} \right) R_L = \frac{1}{2} \left( \frac{V_m}{R_f + R_L} \right) R_L$$

$$V_{rms} = \frac{V_m/2}{1 + \frac{R_f}{R_L}}$$

### Rectifier efficiency

**The ratio of the DC output power to the AC input power supplied to the rectifier.**

denoted by  $\eta_r$ .

$$\eta_r = \frac{P_{dc}}{P_i}$$

- DC output power is given by  $P_{dc} = I_{dc}^2 R_L$   
For half wave rectifier,  $I_{dc}$  is given by  $I_{dc} = \frac{I_m}{\pi}$   
DC output power can be expressed as  $P_{DC} = \frac{I_m^2}{\pi^2} R_L$
- AC input power is given by  $P_i = I_{RMS}^2 (R_f + R_L)$   
For half wave rectifier,  $I_{RMS}$  is given by  $I_{rms} = \frac{I_m}{2}$

Therefore AC input power is  $P_i = \frac{I_m^2}{4} (R_f + R_L)$

- Therefore efficiency can be expressed as

$$\eta_r = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{I_m^2}{4} (R_f + R_L)} = \frac{0.406 R_L}{(R_f + R_L)}$$

$$\eta_r = \frac{0.406}{\frac{(R_f + R_L)}{R_L}} = \frac{0.406}{1 + \frac{R_f}{R_L}}$$

$$\% \eta_r = \frac{40.6}{1 + \frac{R_f}{R_L}}$$

If diode is ideal,  $R_f = 0$  then

$$\% \eta_{r \max} = 40.6$$

### Ripple factor

**The ratio of RMS value of AC component present in the rectified output to the DC component of the rectified output.** It is denoted by  $\gamma$

$$\gamma = \frac{V_{AC}}{V_{DC}}$$

- The output of the rectifier is a pulsating DC and has two component
  - AC component of RMS value  $V_{AC}$
  - DC component  $V_{DC}$
- Total power output is the sum of powers of DC and ac components

$$\left[ \text{total RMS value of rectified output} \right]^2 = [\text{DC value}]^2 + \left[ \text{RMS value of AC component} \right]^2$$

$$V_{RMS}^2 = V_{DC}^2 + V_{AC}^2$$

- Dividing throughout by  $V_{DC}^2$  we get

$$\frac{V_{RMS}^2}{V_{DC}^2} = 1 + \frac{V_{AC}^2}{V_{DC}^2} \quad \text{implies} \quad \left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \left( \frac{V_{AC}}{V_{DC}} \right)^2 \quad | \quad \text{but } \frac{V_{AC}}{V_{DC}} = \gamma$$

$$\left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \gamma^2 \quad \text{rearranging we get} \quad \gamma^2 = \left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1$$

$$\therefore \gamma = \sqrt{\left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1}$$

we know that  $V_{RMS} = \frac{V_m/2}{1 + \frac{R_f}{R_L}}$  and  $V_{DC} = \left( \frac{V_m/\pi}{1 + \frac{R_f}{R_L}} \right)$ , hence by substitution we get

$$\gamma = \sqrt{\left( \frac{\pi}{2} \right)^2 - 1}$$

$$\therefore \gamma_{HWR} = 1.21$$

$$\gamma = 1.21 = \frac{V_{AC}}{V_{DC}}$$

$$V_{ac} = 1.21V_{dc}$$

Clearly we see that in the half wave rectifier the AC or the ripple component is 121% of the DC component, which is much more than the acceptable levels..

**Hence half wave rectifier is NOT recommended for practical applications.**

### Peak Inverse Voltage

**The maximum REVERSE voltage that can be applied for the diode.**

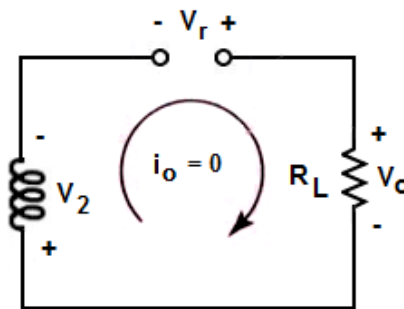


Fig.1.16: Equivalent circuit to find Peak Inverse Voltage

- Applying KVL in the above figure  $v_2 - v_r + i_o R_L = 0$
- since  $i_o = 0$  we infer  $v_r = v_2 = V_m \sin \omega t$

hence **PIV =  $V_{r \max} = V_m$**  when  $\sin \omega t = 1$

For a HWR circuit, as during reverse bias the max voltage appearing across it is the entire secondary voltage – the diode chosen should be such that it can withstand the given value of  $V_m$ , and still operate.

### LINKS TO VIDEOS

*Half wave Rectifier Explained:* [https://www.youtube.com/watch?v=LI0IOk\\_Ltfc](https://www.youtube.com/watch?v=LI0IOk_Ltfc)

### Problems

- A sinusoidal voltage of peak value 40V and frequency 50Hz is applied to a half wave rectifier having a load resistor of  $800\Omega$  and  $R_f$  of the diode is  $8\Omega$ . Calculate

- Peak, DC and RMS value of load current
- DC output power
- ac input power
- rectifier efficiency

Peak current is given by  $I_m = \frac{V_m}{R_f + R_L} = \frac{40}{8 + 800} = 49.5\text{mA}$

DC current is given by  $I_{DC} = \frac{I_m}{\pi} = \frac{49.5\text{m}}{\pi} = 15.75\text{mA}$

RMS current is given by  $I_{rms} = \frac{I_m}{2} = \frac{49.5\text{m}}{2} = 24.75\text{mA}$

DC output power is given by

$$P_{dc} = I_{dc}^2 R_L$$

$$P_{DC} = (15.75\text{m})^2 * 800$$

$$P_{dc} = 198.45\text{mW}$$

AC input power is given by

$$P_i = I_{rms}^2 (R_f + R_L)$$

$$P_i = (24.75\text{m})^2 * (8 + 800)$$

$$P_i = 494.95\text{mW}$$

Rectifier efficiency

$$\eta_r = \frac{P_{dc}}{P_i} * 100\%$$

$$\eta_r = \frac{198.45\text{m}}{494.95\text{m}} * 100\%$$

$$\eta_r = 40.09\%$$

2. The input to a half wave rectifier is given through a 10:1 transformer from a supply of  $230\sin 314t$ . If  $R_f = 50\Omega$  and  $R_L = 500\Omega$  determine

- DC load voltage
- RMS load voltage
- PIV
- rectifier efficiency
- DC power delivered to load
- freq of output waveform

Secondary voltage is given by  $v_2 = \frac{N_2}{N_1} V_m \sin \omega t = \frac{1}{10} * 230\sin 314t$

$$v_2 = 23\sin 314t$$

Frequency of the output waveform is given by  $f = \frac{\omega}{2\pi} = \frac{314}{2\pi} = 50\text{Hz}$

DC load voltage is given by  $V_{DC} = \left( \frac{V_m/\pi}{1 + \frac{R_f}{R_L}} \right) = \frac{23/\pi}{1 + \frac{50}{500}} = 6.66\text{V}$

RMS load voltage is given by  $V_{RMS} = \frac{V_m/2}{1 + \frac{R_f}{R_L}} = \frac{23/2}{1 + \frac{50}{500}} = 10.45\text{V}$

PIV Across the diode is given by  $PIV = V_m = 23\text{V}$

DC output power is given by  $P_{DC} = \frac{V_{DC}^2}{R_L} = \frac{(6.66)^2}{500} \quad P_{dc} = 88\text{mW}$

Rectifier efficiency  $\% \eta_r = \frac{40.6}{1 + \frac{R_f}{R_L}} = \frac{40.6}{1 + \frac{50}{500}} = 36.91$

sketch  $v_i$ ,  $v_d$  and  $i_d$  if the input is sinusoidal of 50 Hz. what if  $V_d$


$= 0.7\text{V}$


$$V_{dc} = \frac{V_m}{\pi} = 2\text{V}$$

$$v_i \text{ peak} = V_m = 2\pi \text{ V}$$

$$i_d \text{ peak} = I_m = \frac{2\pi}{2.5} = 2.51 \text{ mA}$$

$$v_d = 0, \text{ diode is ideal}$$

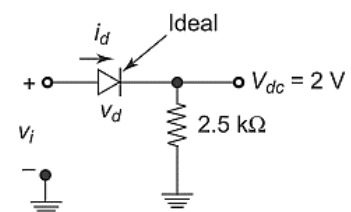

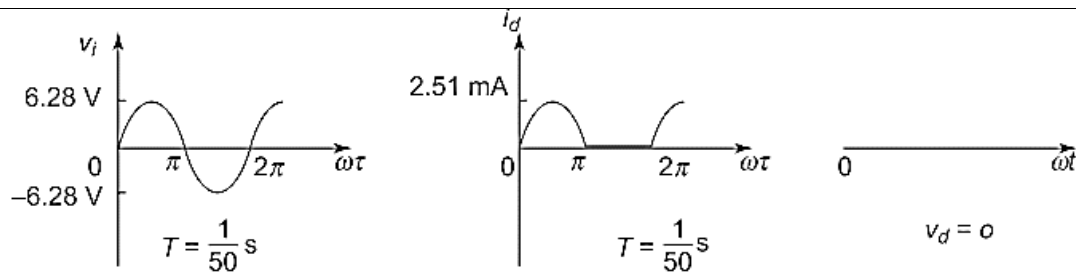

if the diode has  $V_T = 0.7$  V.

$v_d = \frac{V_m - V_T}{\pi} = 2$  V, it is an approximation as output voltage is not exactly sinusoidal.

$v_i$  peak  $= V_m = 2\pi + 0.7 = 6.98$  V


For  $v_i < V_T = 0.7$  V,  $i_d = 0$  at time  $t_1$ ,

$$6.98 \sin 2\pi f t_1 = 0.7 \text{ V,}$$

$$t_1 = 0.0011 \text{ s}$$

$$i_d \text{ peak, } I_m = \frac{V_m - V_T}{2.5} = \frac{2\pi}{2.5} = 2.51 \text{ mA}$$

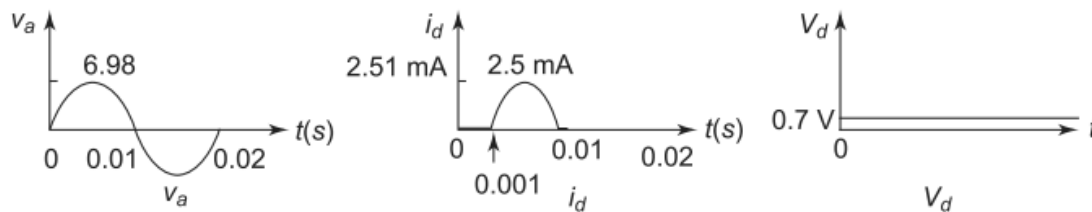$v_i$  in sinusoidal with peak 6.98 V,  $f = 50$  Hz



### 5. For a sinusoidal input of 10 V peak, sketch $i_R$ and $v_o$ in the network

For Si,  $V_T = 0.7$  V

During positive half-cycle, the diode does not conduct up to 0.7 V.

$$v_i \Rightarrow 0 - 0.7 \text{ V}$$

$$v_o = \left( \frac{9}{10} \right) v_i$$

$$= 0.9 v_i \text{ up to } 0.7 \text{ V}$$

$$i_R = 0.1 v_i \text{ up to } 0.07 \text{ mA}$$

For  $v_i \geq 0.7$  V, diode voltage remains constant on both halves of the cycle.

$$v_o = 0.7 \text{ V,}$$

$$i_R = \frac{v_i - 0.7}{1}$$



$$= (v_i - 0.7) \text{ mA}$$


$$i_R (\text{peak}) = (10 - 0.7) = 9.3 \text{ mA}$$

During negative half-cycle, the diode open circuits

$$i_R (\text{peak}) = \frac{10}{1} = 10 \text{ mA}$$
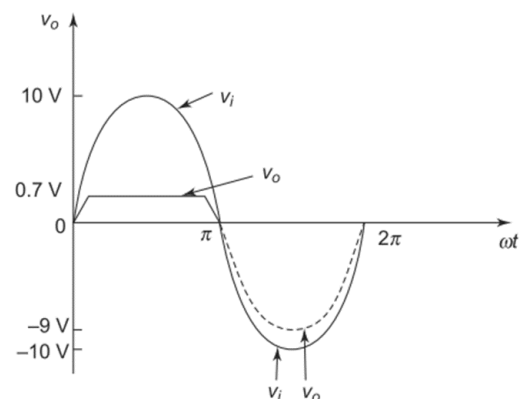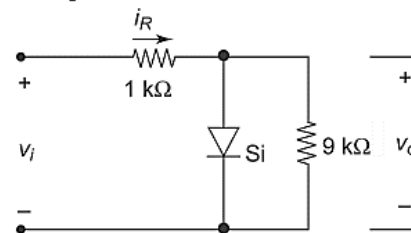
$$v_o = 0.9 v_i \text{ peak} = 9 \text{ V}$$



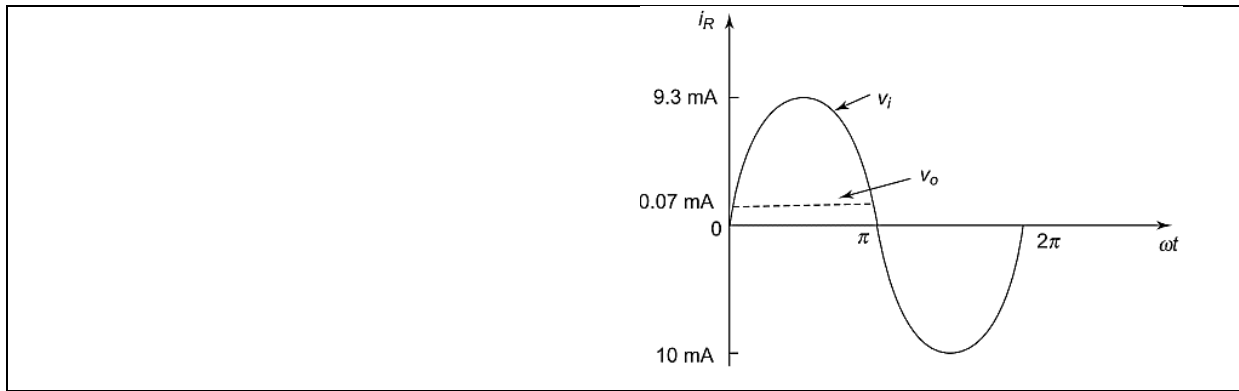

### LINKS TO VIDEOS

Introduction to Rectifier : <https://www.youtube.com/watch?v=Xmu31a-59vw>

Half Wave Rectifier (HWR) : [https://www.youtube.com/watch?v=AspBbh\\_j0uk](https://www.youtube.com/watch?v=AspBbh_j0uk)

RMS Load Voltage and Current : <https://www.youtube.com/watch?v=XTfWAYuyfVU>

Ripple Factors (RF): [https://www.youtube.com/watch?v=SgK\\_kyIibrk&t=152s](https://www.youtube.com/watch?v=SgK_kyIibrk&t=152s)

Efficiency and PIV: <https://www.youtube.com/watch?v=XLbtAmcXYKA>

### Full wave rectifier - center-tapped – operation and waveforms

- The step down transformer reduces the AC supply voltage to the required level and the AC voltage to be rectified is applied across the primary of the transformer such that the voltage across the secondary is available for rectification.
- Full-wave rectifier rectifies both cycles of the ac input.
- Let **voltage applied across the primary** of the transformer be  **$v_1 = V_m \sin \omega t$**  where  **$V_m$**  is the peak value
- The voltage across the secondary of the transformer available for rectification is given by  **$v_2 = \frac{N_2}{N_1} V_m \sin \omega t$**  where  $\frac{N_2}{N_1}$  is the turns ratio of the transformer
- If  $N_2 = N_1$   **$v_2 = V_m \sin \omega t$**

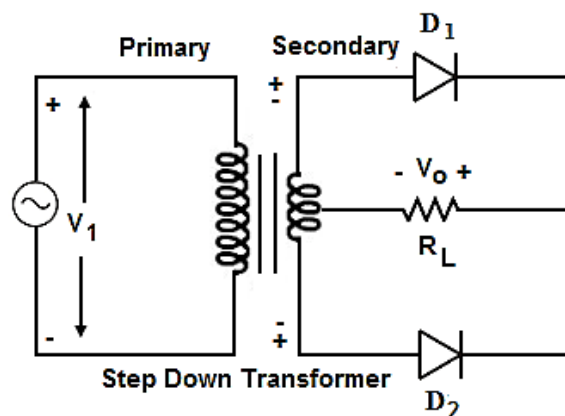


Fig.1.17: Full-wave rectifier



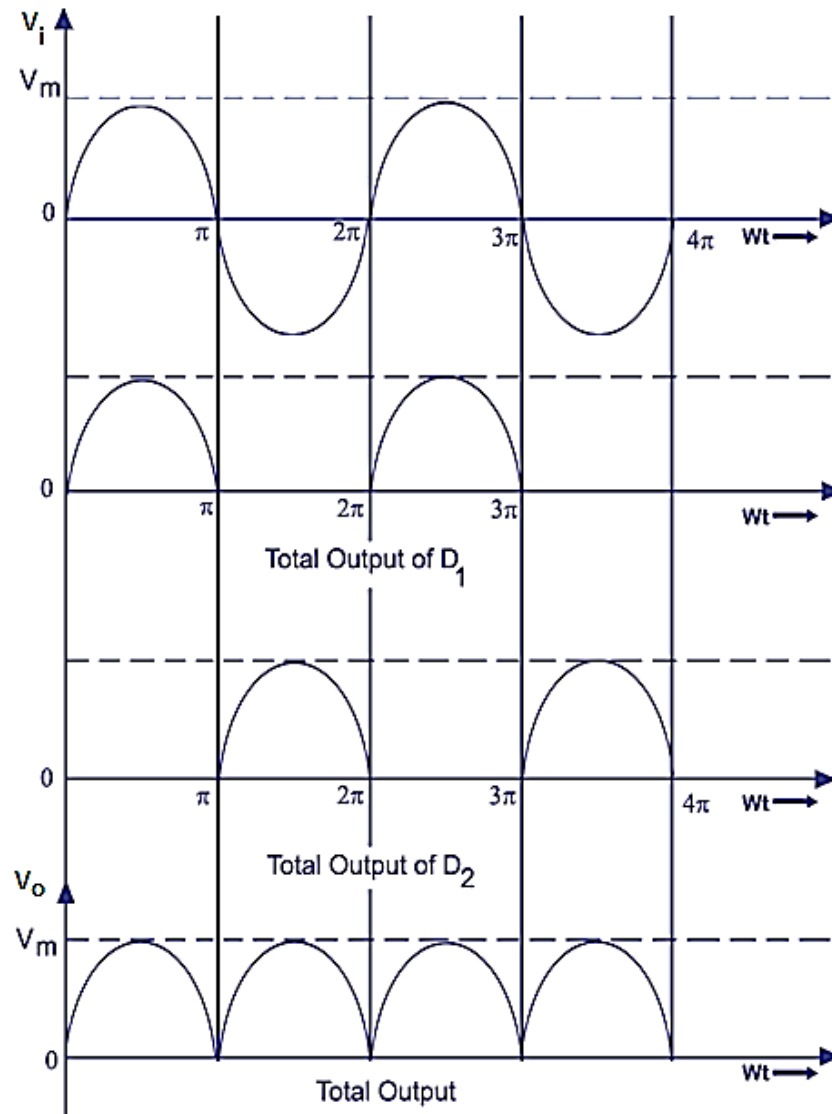


Fig.1.17: Full-wave rectifier waveform

- During the **positive half cycle diode D<sub>1</sub> conducts** and **diode D<sub>2</sub> remains OFF** and the current  $i_o = i_{D1}$  flows through the load. The load voltage  $v_o = i_o R_L$ .
- During the **negative half cycle diode D<sub>2</sub> conducts** and **diode D<sub>1</sub> remains OFF** and the current  $i_o = i_{D2}$  flows through the load. The load voltage  $v_o = i_o R_L$ .

Hence during a total cycle the output waveform has 2 positive sinusoidal waveforms as opposed to just one in a half wave rectifier HWR

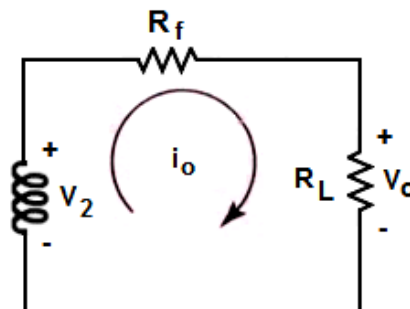


Fig.1.18: Equivalent circuit to find full-wave rectifier current

From the circuit shown in the Fig.1.18

$$i_o = \frac{v_2}{R_f + R_L} = \frac{V_m \sin \omega t}{R_f + R_L}$$

$$i_o = I_m \sin \omega t \quad \text{Where } I_m = \frac{V_m}{R_f + R_L} \text{ is the peak load current}$$

### Average DC load current

$$I_{dc} = \frac{\text{Area under one cycle of } i_o}{\text{Period of } i_o}$$

$$I_{DC} = \int_0^\pi \frac{i_o d\omega t}{\pi} = \frac{1}{\pi} \int_0^\pi I_m \sin \omega t d\omega t$$

$$I_{DC} = \frac{I_m}{\pi} [-\cos \omega t]_0^\pi$$

$$I_{dc} = \frac{2I_m}{\pi}$$

### Average DC load voltage

$$V_{dc} = I_{dc} R_L$$

$$V_{DC} = \left( \frac{2I_m}{\pi} \right) R_L = \frac{2}{\pi} \left( \frac{V_m}{R_f + R_L} \right) R_L$$

$$V_{dc} = \frac{2V_m}{\pi} \left( \frac{R_L}{R_f + R_L} \right) = \left( \frac{2V_m/\pi}{\frac{R_f + R_L}{R_L}} \right)$$

$$V_{dc} = \left( \frac{2V_m/\pi}{1 + \frac{R_f}{R_L}} \right)$$

### RMS load current

$$I_{RMS} = \sqrt{\frac{\text{Area under one cycle of } i_o^2}{\text{Period of } i_o}}$$

$$I_{RMS} = \sqrt{\frac{1}{\pi} \int_0^\pi i_o^2 d\omega t} = \sqrt{\frac{1}{\pi} \int_0^\pi I_m^2 \sin^2 \omega t d\omega t}$$

$$I_{RMS} = I_m \sqrt{\frac{1}{\pi} \int_0^\pi \frac{1}{2} (1 - \cos 2\omega t) d\omega t}$$

$$I_{RMS} = I_m \sqrt{\frac{1}{2\pi} \left[ \int_0^\pi d\omega t - \int_0^\pi \cos 2\omega t d\omega t \right]}$$

$$I_{RMS} = I_m \sqrt{\frac{1}{2\pi} \left[ (\omega t)_0^\pi - \left( \frac{\sin 2\omega t}{2} \right)_0^\pi \right]}$$

$$I_{\text{RMS}} = I_m \sqrt{\frac{1}{2\pi} \left[ (\pi - 0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]} = I_m \sqrt{\frac{1}{2\pi} \left[ (\pi) - \frac{1}{2} (0) \right]} = I_m \sqrt{\frac{\pi}{2\pi}}$$

$$I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$$

### RMS load voltage

$$V_{\text{RMS}} = I_{\text{RMS}} R_L$$

$$V_{\text{RMS}} = \left( \frac{I_m}{\sqrt{2}} \right) R_L = \frac{1}{\sqrt{2}} \left( \frac{V_m}{R_f + R_L} \right) R_L$$

$$V_{\text{RMS}} = \frac{V_m / \sqrt{2}}{1 + \frac{R_f}{R_L}}$$

### Rectifier efficiency

**The ratio of the DC output power to the AC input power supplied to the rectifier.**  
denoted by  $\eta_r$ .

$$\eta_r = \frac{P_{\text{dc}}}{P_i}$$

DC output power is given by  $P_{\text{DC}} = I_{\text{DC}}^2 R_L$

For Full wave rectifier,  $I_{\text{DC}}$  is given by  $I_{\text{DC}} = \frac{2I_m}{\pi}$

Hence DC output power becomes  $P_{\text{DC}} = \frac{4I_m^2}{\pi^2} R_L$

AC input power is given by  $P_i = I_{\text{RMS}}^2 (R_f + R_L)$

For full wave rectifier,  $I_{\text{RMS}}$  is given by  $I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$

AC input power is hence :  $P_i = \frac{I_m^2}{2} (R_f + R_L)$

Rectification efficiency hence becomes

$$\eta_r = \frac{\frac{4I_m^2}{\pi^2} R_L}{\frac{I_m^2}{2} (R_f + R_L)} = \frac{8}{\pi^2} \frac{R_L}{(R_f + R_L)} = \frac{0.812}{\frac{(R_f + R_L)}{R_L}} = \frac{0.812}{1 + \frac{R_f}{R_L}}$$

$$\% \eta_r = \frac{81.2}{1 + \frac{R_f}{R_L}}$$

If diode are ideal,  $R_f = 0$  then  $\% \eta_{r \text{ max}} = 81.2$

### Ripple factor

**The ratio of RMS value of AC component present in the rectified output to the DC component of the rectified output.** It is denoted by  $\gamma = \frac{V_{\text{AC}}}{V_{\text{DC}}}$

The output of the rectifier is a pulsating DC and has two component

1. AC component of RMS value  $V_{AC}$

2. DC component  $V_{DC}$

Total power output is the sum of powers of DC and ac components

$$\left[ \begin{array}{c} \text{total RMS value of} \\ \text{rectified output} \end{array} \right]^2 = [\text{DC value}]^2 + \left[ \begin{array}{c} \text{RMS value of} \\ \text{AC component} \end{array} \right]^2$$

$$V_{RMS}^2 = V_{DC}^2 + V_{AC}^2$$

Dividing throughout by  $V_{DC}^2$  we get

$$\frac{V_{RMS}^2}{V_{DC}^2} = 1 + \frac{V_{AC}^2}{V_{DC}^2} \quad \text{implies} \quad \left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \left( \frac{V_{AC}}{V_{DC}} \right)^2 \quad | \quad \text{but } \frac{V_{AC}}{V_{DC}} = \gamma$$

$$\left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \gamma^2 \quad \text{rearranging we get} \quad \gamma^2 = \left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1$$

$$\therefore \gamma = \sqrt{\left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1}$$

We know that.  $V_{RMS} = \frac{V_m/\sqrt{2}}{1 + \frac{R_f}{R_L}}$  and  $V_{DC} = \left( \frac{2V_m/\pi}{1 + \frac{R_f}{R_L}} \right)$  substituting these

values in the equation we get  $\gamma = \sqrt{\left( \frac{\pi}{2\sqrt{2}} \right)^2 - 1}$

$$\gamma = 0.483$$

$$\gamma = 0.483 = \frac{V_{AC}}{V_{DC}} \quad \text{hence} \quad V_{AC} = 0.483V_{DC}$$

INFERENCE :

In full wave rectifier the ripple component is 48.3% of the DC component. As the ripple content is less THAN the DC value **FWR gives more DC output voltage than a HWR**

### Peak Inverse Voltage

**the maximum reverse voltage that can be applied for the diode.**

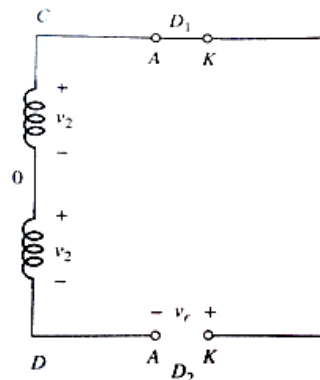


Fig.1.19: Equivalent circuit to find Peak Inverse Voltage

- Applying KVL to the circuit in Fig.1.19, we get,  $v_2 + v_2 - v_r = 0$  where  $v_2 = V_m \sin \omega t$

$$\text{hence } v_r = 2v_2 = 2V_m \sin \omega t$$

$$\boxed{PIV = v_{r \max} = 2V_m} \quad \text{when } \sin \omega t = 1$$

- For a center tapped circuit, if any one diode doesn't conduct during reverse bias the max voltage appearing across it is **2 times the entire secondary voltage** – the diode chosen should be such that it can withstand the given value of  $2 \cdot V_m$ , **which is VERY MUCH below its PIV** and still operate, which is difficult to do .
- This is a draw back of centre tapped transformer based FWR

### Full wave bridge rectifier – operation and waveform

- Fig.1.20 shows the circuit diagram of a full wave bridge rectifier. It uses **FOUR** diodes connected in the form of a bridge.
- The AC voltage to be rectified is applied across primary of the transformer and the voltage across the secondary is available for rectification.
- Full wave bridge rectifier rectifies BOTH cycles of the AC input.
- Let the voltage applied across the primary of the transformer be  $v_1 = V_m \sin \omega t$   
where  $V_m$  is the peak value
- The voltage across the secondary of the transformer available for rectification is given by  $v_2 = \frac{N_2}{N_1} V_m \sin \omega t$  where  $\frac{N_2}{N_1}$  is the turns ratio of the transformer
- If  $N_2 = N_1$   $v_2 = V_m \sin \omega t$

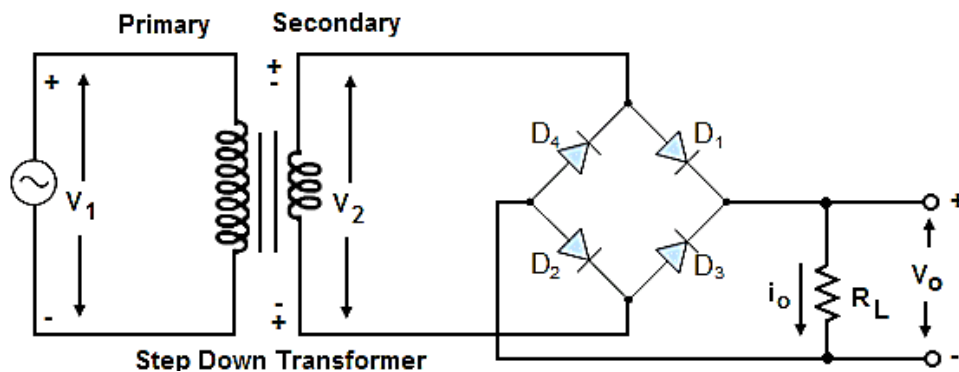


Fig.1.20: Full-wave bridge rectifier

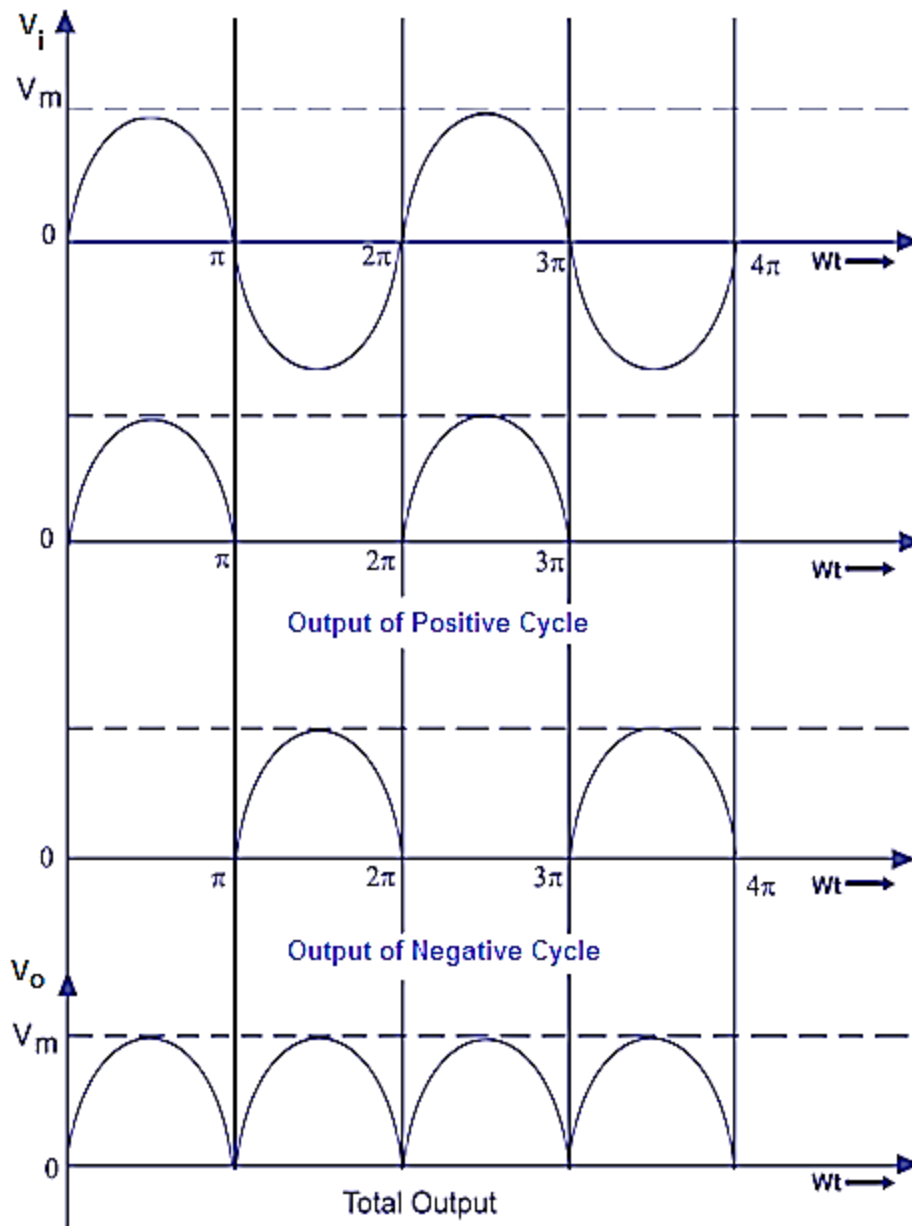


Fig.1.21: Full-wave bridge rectifier waveform

- During the **positive half cycle the diode  $D_1$  and  $D_2$  are forward biased** and  **$D_3$  and  $D_4$  are reverse biased** and the current  $i_o = i_{D1} = i_{D2}$  flows through the load. The load voltage  $v_o = i_o R_L$ .

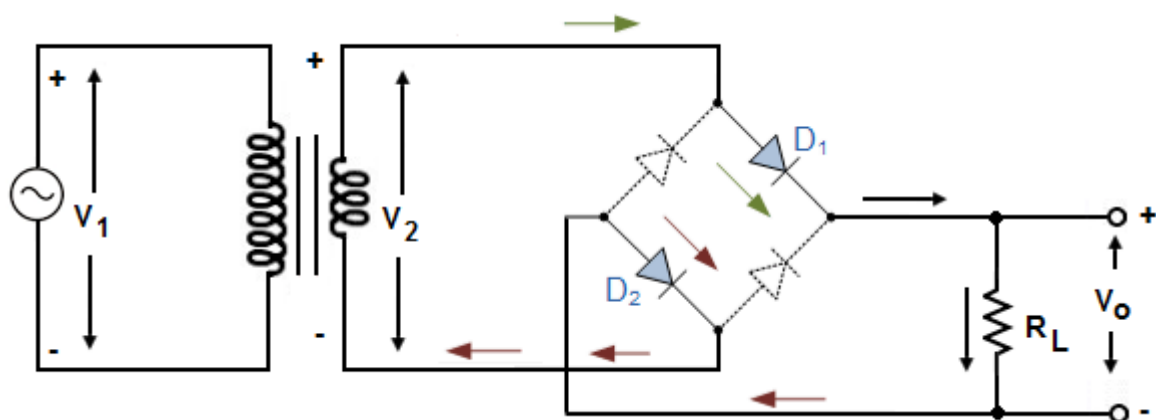


Fig.1.22: Equivalent circuit during positive cycle

- During the **negative half cycle the diode D<sub>3</sub> and D<sub>4</sub> are forward biased** and **D<sub>1</sub> and D<sub>2</sub> are reverse biased** and the **current  $i_o = i_{D3} = i_{D4}$**  flows through the load. The load voltage  $v_o = i_o R_L$ .

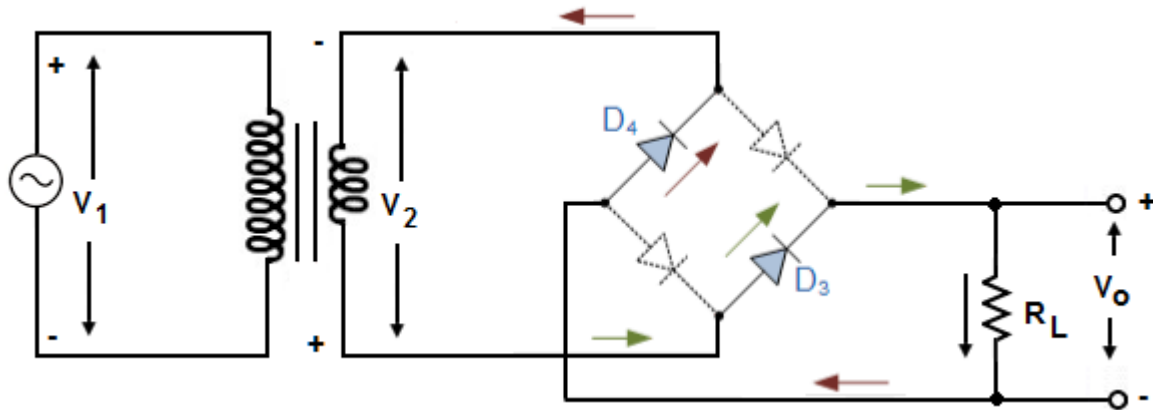


Fig.1.23: Equivalent circuit during negative cycle

- Applying KVL to the circuit shown in Fig.1.22, we get

$$-v_2 + i_o R_f + i_o R_L + i_o R_f = 0$$

$i_o(2R_f + R_L) = v_2$  re arranging and substituting for  $v_2$ , we get

$$i_o = \frac{V_m \sin \omega t}{2R_f + R_L} \quad i_o = I_m \sin \omega t \quad \text{where } I_m = \frac{V_m}{2R_f + R_L} \text{ is the peak load current}$$

#### Average DC load current

$$I_{DC} = \frac{\text{Area under one cycle of } i_o}{\text{Period of } i_o}$$

$$I_{DC} = \int_0^\pi \frac{i_o d\omega t}{\pi}$$

$$I_{DC} = \frac{1}{\pi} \int_0^\pi I_m \sin \omega t d\omega t = \frac{I_m}{\pi} [-\cos \omega t]_0^\pi$$

$$I_{DC} = \frac{2I_m}{\pi}$$

#### Average DC load voltage

$$V_{DC} = I_{DC} R_L$$

$$V_{DC} = \left( \frac{2I_m}{\pi} \right) R_L = \frac{2}{\pi} \left( \frac{V_m}{2R_f + R_L} \right) R_L$$

$$V_{DC} = \frac{2V_m}{\pi} \left( \frac{R_L}{2R_f + R_L} \right) = \frac{2V_m}{\pi} \left( \frac{1}{\frac{2R_f + R_L}{R_L}} \right)$$

$$V_{DC} = \left( \frac{2V_m/\pi}{1 + \frac{2R_f}{R_L}} \right)$$

**RMS load current**

$$I_{\text{RMS}} = \sqrt{\frac{\text{Area under one cycle of } i_o^2}{\text{Period of } i_o}}$$

$$I_{\text{RMS}} = \sqrt{\frac{\int_0^\pi i_o^2 d\omega t}{\pi}}$$

$$I_{\text{RMS}} = \sqrt{\frac{\int_0^\pi I_m^2 \sin^2 \omega t d\omega t}{\pi}} = I_m \sqrt{\frac{1}{\pi} \int_0^\pi \frac{1}{2} (1 - \cos 2\omega t) d\omega t} \quad \text{as WKT } \sin^2 \omega t = \frac{1}{2} (1 - \cos 2\omega t)$$

$$I_{\text{RMS}} = I_m \sqrt{\frac{1}{2\pi} \left[ \int_0^\pi d\omega t - \int_0^\pi \cos 2\omega t d\omega t \right]}$$

$$I_{\text{RMS}} = I_m \sqrt{\frac{1}{2\pi} \left[ \omega t \Big|_0^\pi - \frac{\sin 2\omega t}{2} \Big|_0^\pi \right]}$$

$$I_{\text{RMS}} = I_m \sqrt{\frac{1}{2\pi} \left[ (\pi - 0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]}$$

$$I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$$

**RMS load voltage**

$$V_{\text{RMS}} = I_{\text{RMS}} R_L$$

$$V_{\text{RMS}} = \left( \frac{I_m}{\sqrt{2}} \right) R_L = \frac{1}{\sqrt{2}} \left( \frac{V_m}{2R_f + R_L} \right) R_L$$

$$V_{\text{RMS}} = \frac{V_m / \sqrt{2}}{1 + \frac{2R_f}{R_L}}$$

**Rectifier efficiency**

**The ratio of the DC output power delivered to the load to the AC input power supplied from the secondary of the transformer.** It is denoted by  $\eta_r = \frac{P_{\text{DC}}}{P_i}$

- DC output power is given by  $P_{\text{DC}} = I_{\text{DC}}^2 R_L$

For full wave rectifier,  $I_{\text{DC}}$  is given by  $I_{\text{DC}} = \frac{2I_m}{\pi}$

Hence DC output power :  $P_{\text{DC}} = \frac{4I_m^2}{\pi^2} R_L$

- AC input power is given by  $P_i = I_{\text{RMS}}^2 (2R_f + R_L)$

For full wave rectifier,  $I_{\text{RMS}}$  is given by  $I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$

Hence AC input power can be expressed as  $P_i = \frac{I_m^2}{2} (2R_f + R_L)$



- Therefore efficiency can be expressed as  $\eta_r = \frac{\frac{4I_m^2 R_L}{\pi^2}}{\frac{I_m^2}{2}(2R_f + R_L)} = \frac{8}{\pi^2} \frac{R_L}{(2R_f + R_L)}$

$$\eta_r = \frac{0.812}{\frac{(2R_f + R_L)}{R_L}} = \frac{0.812}{1 + \frac{2R_f}{R_L}}$$

$$\% \eta_r = \frac{81.2}{1 + \frac{2R_f}{R_L}}$$

- If diodes are ideal,  $R_f = 0$  then  $\% \eta_{r \max} = 81.2$

### Ripple factor

**The ratio of RMS value of AC component present in the rectified output to the DC component of the rectified output.** It is denoted by  $\gamma = \frac{V_{AC}}{V_{DC}}$

- The output of the rectifier is a pulsating DC and has two component
  - AC component of RMS value  $V_{AC}$
  - DC component  $V_{DC}$
- Total power output is the sum of powers of DC and AC components

$$\left[ \begin{array}{c} \text{total RMS value of} \\ \text{rectified output} \end{array} \right]^2 = [\text{DC value}]^2 + \left[ \begin{array}{c} \text{RMS value of} \\ \text{AC component} \end{array} \right]^2$$

$$V_{RMS}^2 = V_{DC}^2 + V_{AC}^2$$

- Dividing throughout by  $V_{DC}^2$  we get

$$\frac{V_{RMS}^2}{V_{DC}^2} = 1 + \frac{V_{AC}^2}{V_{DC}^2} \quad \text{implies} \quad \left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \left( \frac{V_{AC}}{V_{DC}} \right)^2 \quad | \quad \text{but } \frac{V_{AC}}{V_{DC}} = \gamma$$

$$\left( \frac{V_{RMS}}{V_{DC}} \right)^2 = 1 + \gamma^2 \quad \text{re arranging we get} \quad \gamma^2 = \left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1$$

$$\therefore \gamma = \sqrt{\left( \frac{V_{RMS}}{V_{DC}} \right)^2 - 1}$$

$$V_{RMS} = \frac{V_m/\sqrt{2}}{1 + \frac{2R_f}{R_L}} \quad \& \quad V_{DC} = \left( \frac{2V_m/\pi}{1 + \frac{2R_f}{R_L}} \right)$$

- Therefore  $\gamma = \sqrt{\left( \frac{\pi}{2\sqrt{2}} \right)^2 - 1} = 0.483$

$$\gamma = 0.483 = \frac{V_{AC}}{V_{DC}}$$

$$V_{AC} = 0.483 V_{DC}$$

INFERENCE :

In full wave rectifier the ripple component is 48.3% of the DC component. As the ripple content is less THAN the DC value **FWR gives more DC output voltage than a HWR**

## Peak Inverse Voltage

**The maximum reverse voltage that can be applied TO the diode.**

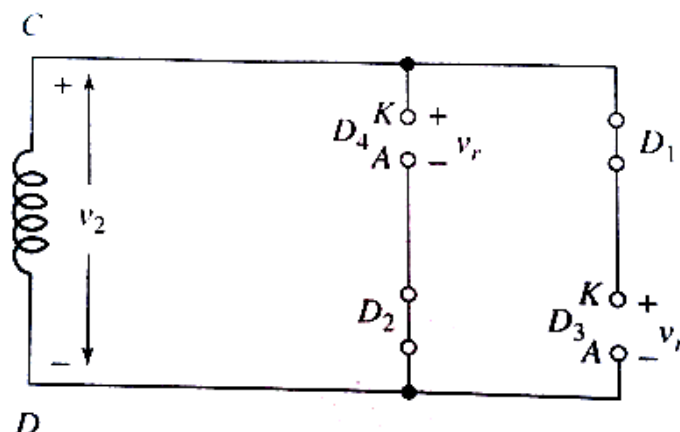


Fig.1.23: Equivalent circuit to find Peak Inverse Voltage

- Applying KVL to the circuit in Fig.1.23 we get,  $v_2 - v_r = 0$  where  $v_2 = V_m \sin \omega t$  hence  $v_r = v_2 = V_m \sin \omega t$  **PIV =  $v_{r \max} = V_m$  when  $\sin \omega t = 1$**
- The diode chosen should be such that it can withstand the given value of  $V_m$ , **which is VERY MUCH below its PIV** and still operate.

## Comparison of rectifiers

Parameter	Have-wave Rectifier	Full-wave centre tapped - Rectifier	Full-wave Bridge Rectifier
Peak Current $I_m$	$\frac{V_m}{R_f + R_L}$	$\frac{V_m}{R_f + R_L}$	$\frac{V_m}{2R_f + R_L}$
DC load Current $I_{DC}$	$\frac{I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$
RMS load Current $I_{RMS}$	$\frac{I_m}{2}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$
DC load Voltage $V_{DC}$	$\frac{V_m/\pi}{1 + \frac{R_f}{R_L}}$	$\frac{2V_m/\pi}{1 + \frac{R_f}{R_L}}$	$\frac{2V_m/\pi}{1 + \frac{2R_f}{R_L}}$
RMS load Voltage $V_{RMS}$	$\frac{V_m/2}{1 + \frac{R_f}{R_L}}$	$\frac{V_m/\sqrt{2}}{1 + \frac{R_f}{R_L}}$	$\frac{V_m/\sqrt{2}}{1 + \frac{2R_f}{R_L}}$
Efficiency $\eta_r$	$\frac{0.406}{1 + \frac{R_f}{R_L}}$	$\frac{0.812}{1 + \frac{R_f}{R_L}}$	$\frac{0.812}{1 + \frac{2R_f}{R_L}}$
Ripple Factor $\gamma$	1.21	0.483	0.483
Peak Inverse Voltage PIV	$V_m$	$2V_m$	$V_m$

**LINKS TO VIDEOS:**

Half wave Rectifier Explained: [https://www.youtube.com/watch?v=L10IOk\\_Ltfc](https://www.youtube.com/watch?v=L10IOk_Ltfc)

Full wave Rectifier Explained: <https://www.youtube.com/watch?v=74QrYyYsftY>

Full Wave Bridge Rectifier: <https://www.youtube.com/watch?v=Kl8IOESVWIM>

Full Wave Center-Tapped Rectifier: <https://www.youtube.com/watch?v=CGZ0yHaAmjs>

Full Wave Rectifier (DC Load Current & Load Voltage):

<https://www.youtube.com/watch?v=XI4mHDveD7g>

PROBLEM: RMS AND DC VALUES IN HWR, FWR: <https://www.youtube.com/watch?v=A2SMI31EgMA>

Calculation of Ripple Factor and Ripple Voltage for HWR and FWR:

<https://www.youtube.com/watch?v=ruEYtTYePRk>

PROBLEM: DIODE RECTIFIER CIRCUITS : <https://www.youtube.com/watch?v=UQVAFcCLoKo>

**Capacitor filter circuit**

- Capacitor filter is used to reduce the ripple content present in the rectified output. It is done by connecting a capacitor in parallel with  $R_L$ .
- Fig.1.24 shows the half wave rectifier with capacitor filter.

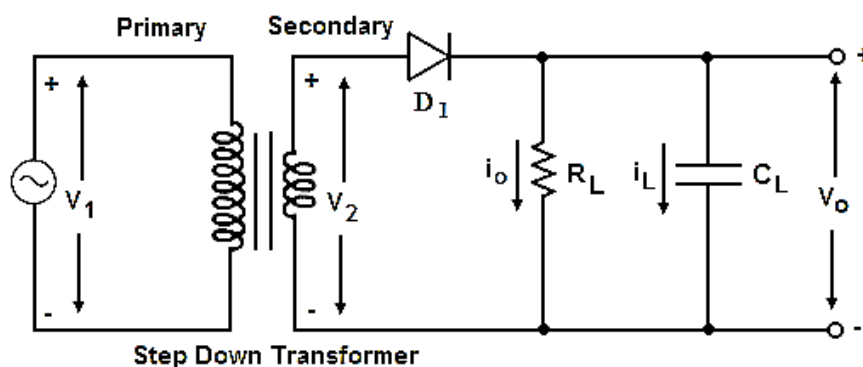


Fig.1.24: Half-wave rectifier with capacitor filter

- During positive half cycle of the AC supply, the diode conducts (on state) and charges the capacitor to the peak value of  $V_m$  of the transformer secondary voltage.
- When the transformer secondary voltage falls below  $V_m$  the diode stops conducting (OFF state).
- As a result, capacitor discharges through  $R_L$  and the voltage on capacitor decreases.

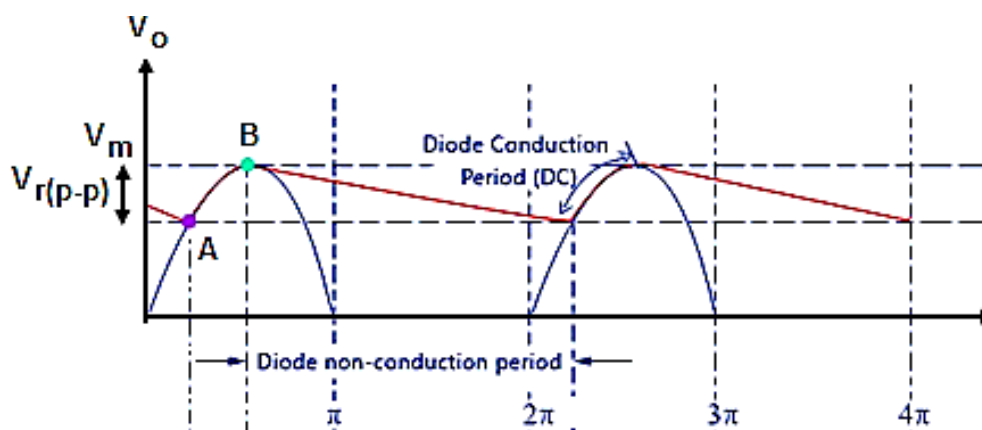


Fig.1.25: Output voltage waveform of Half-wave rectifier with and without capacitor filter

- The capacitor **discharges until the diode starts conducting again** and charges the capacitor in the next positive half-cycle of AC supply.

$V_{r(p-p)}$  is peak-peak ripple voltage on capacitor

$t_c$  is charging time of capacitor

$t_d$  is discharging time of capacitor

$T = t_c + t_d$  time period of output waveform

- In the Fig.1.25 the dotted line shows the **output of the rectifier without capacitor filter**, where  $V_o$  varies between **zero and  $V_m$** .
- When the filter is connected the output  $V_o$  varies between  **$V_m - V_{r(p-p)}$  and  $V_m$** .
- Similarly the waveform obtained from a full-wave rectifier with capacitor filter is as shown in the Fig.1.27.

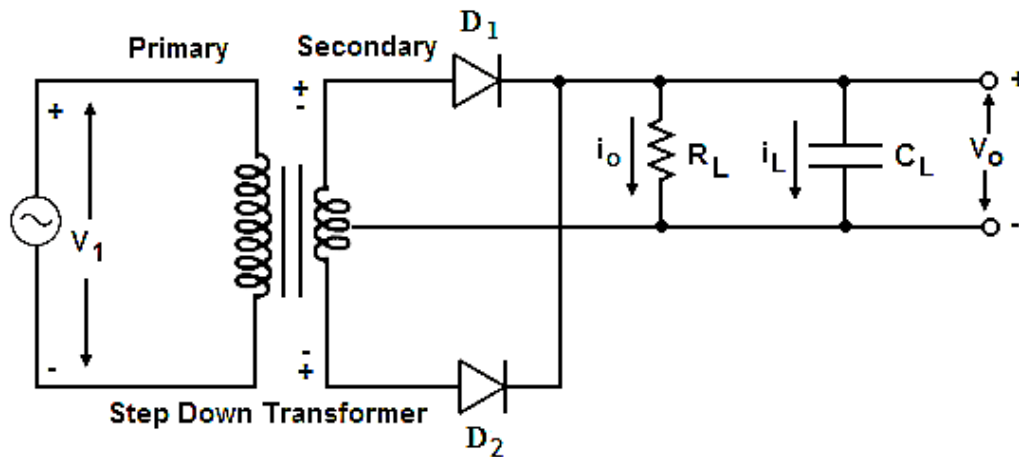


Fig.1.26: Full-wave rectifier with capacitor filter

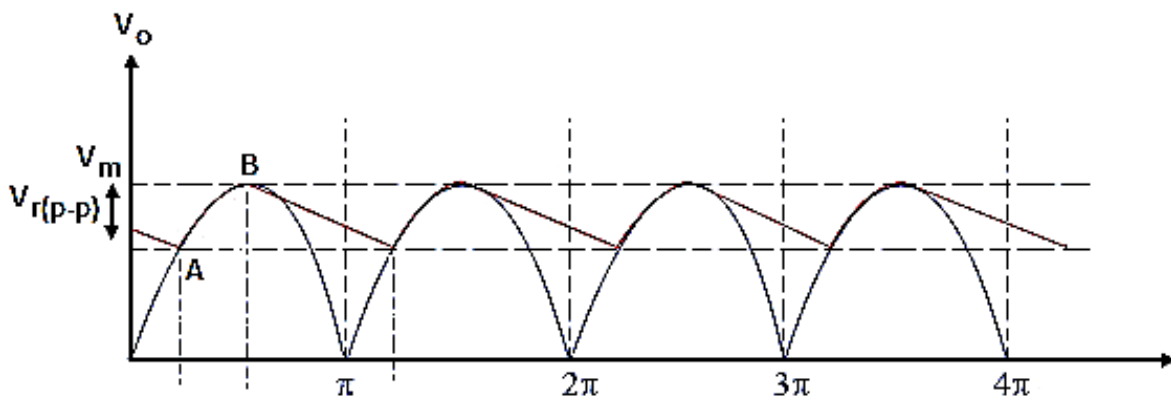


Fig.1.27: Output voltage waveform of full-wave rectifier with and without capacitor filter

- Similarly the waveform obtained from a full-wave bridge rectifier with capacitor filter is as shown in the Fig.1.29.

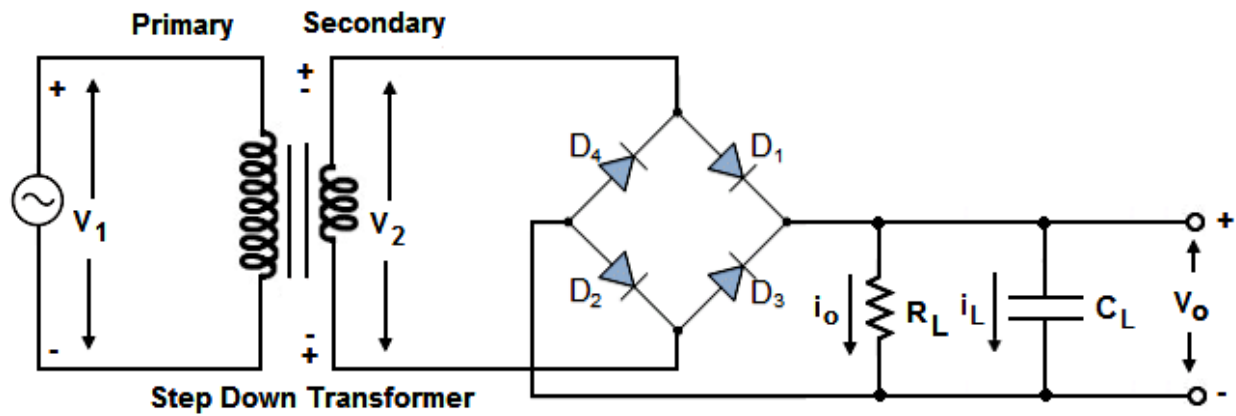


Fig.1.28: Full-wave bridge rectifier with capacitor filter


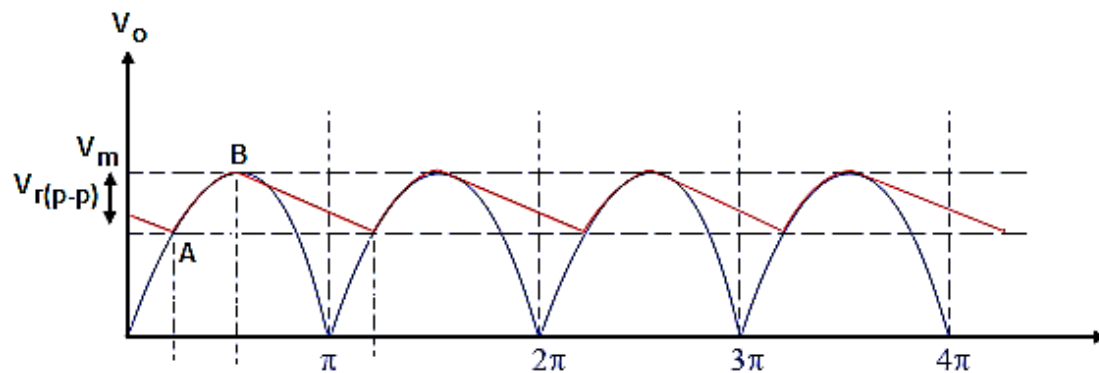


Fig.1.29: Output voltage waveform of full-wave bridge rectifier with and without capacitor filter

[Links TO VIDEOS:](#)

[Peak Detector Circuit Explained : https://www.youtube.com/watch?v=w4531AVjBYY](https://www.youtube.com/watch?v=w4531AVjBYY)

## Zener diode voltage regulator

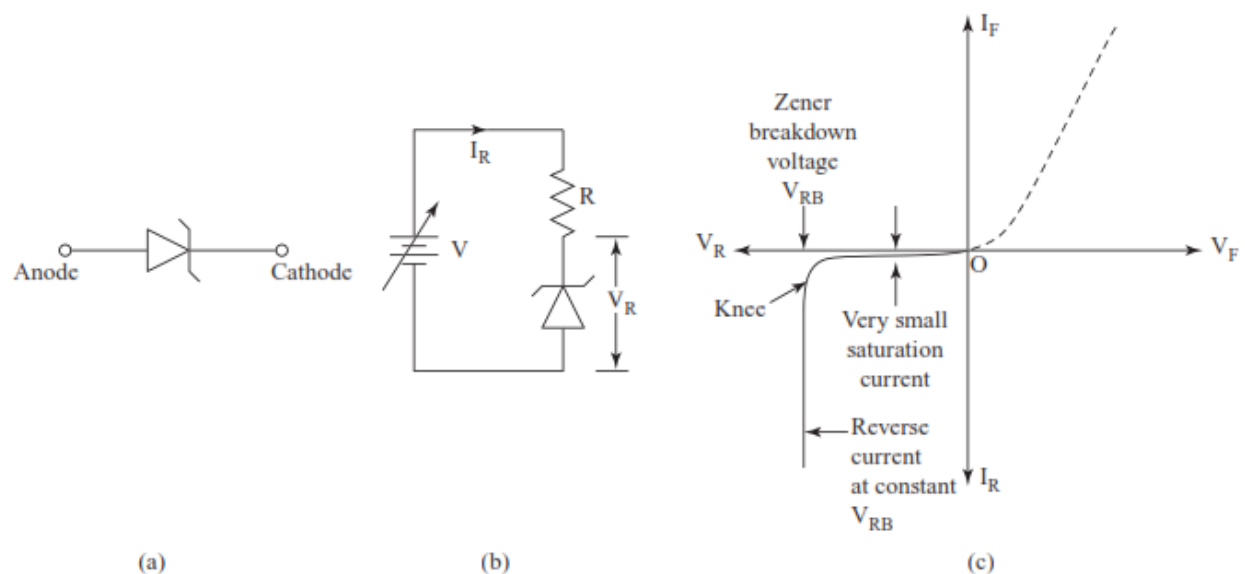

(a) Symbol of a zener diode; (b) zener diode circuit; (c) V-I characteristic

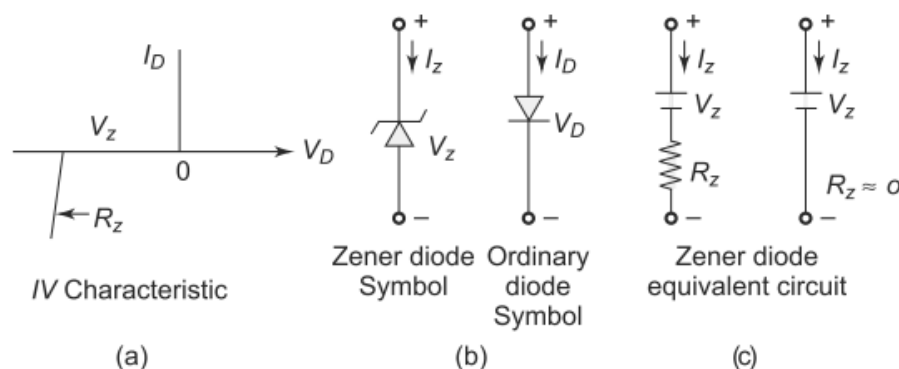


Figure 1 Zener diode equivalent representation

- The output of a rectifier with capacitor filter varies with the changes in the load current and line voltage hence it is called as variable DC or unregulated DC.
- A voltage regulator **is a circuit which accepts unregulated DC input and provides a constant DC output voltage irrespective of the changes in the load current and line voltage** as shown in Fig.1.30.
- Zener diode **operates in the reverse break down region** and has a **constant voltage  $V_Z$**  across its terminal.
- The input voltage  **$V_i$  must be greater than the zener breakdown voltage  $V_Z$** .

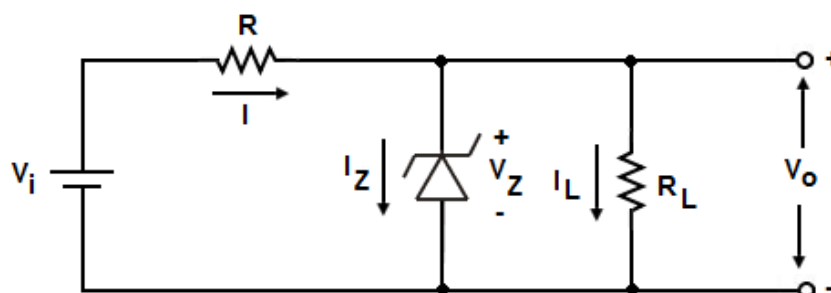


Fig.1.30: Zener diode voltage regulator

- Voltage across  $R_L$  is equal to the voltage across the zener diode since  $R_L$  and zener diode are in parallel.  $V_o = V_Z$
- From the Figure supply current  $I = I_Z + I_L$   
re arranging we have  $I_Z = I - I_L$

- Supply current can also be expressed as

$$I = \frac{V_i - V_o}{R}$$

- Therefore current through the zener diode can be expressed as

$$I_Z = \frac{V_i - V_o}{R} - I_L$$

- $V_i$  varies between  $V_{i_{\min}}$  and  $V_{i_{\max}}$  and  $I_L$  varies between  $I_{L_{\min}}$  and  $I_{L_{\max}}$ . Therefore minimum current through the zener diode is given by

$$\frac{V_{i_{\min}} - V_o}{R} - I_{L_{\max}} > I_{Z_{\min}}$$

- Maximum current through the zener diode is given by

$$\frac{V_{i_{\max}} - V_o}{R} - I_{L_{\min}} < I_{Z_{\max}}$$

- Maximum allowable power dissipation in the Zener is

$$P_D = I_{L_{\max}} V_Z$$

## LINKS TO VIDEOS:

*Introduction to Zener Diodes:* <https://www.youtube.com/watch?v=JdL3DnnFHXw>

*Effects of Temperature on Zener Voltage* <https://www.youtube.com/watch?v=Jffjpym7K8Y>


*ZENER DIODE REGULATOR (PART 1):* <https://www.youtube.com/watch?v=6xGCOrPBL4s>

## Problem

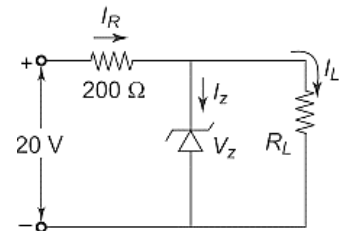1.

For  $V_Z=10V$ ,  $R_Z=0$ ;  $P_{Z_{\max}}=350mW$ , find the following:

- For  $R_L = 180 \Omega$ , determine all currents and voltages.
- Repeat part (a) for  $R_L = 450 \Omega$ .
- Find the value of  $R_L$  for the zener to draw maximum power.
- Find the minimum value of  $R_L$  for the zener to be just in on-state.



a) Find  $I_R$ ,  $I_L$ ,  $I_Z$  and  $V_Z$

As  $R_L$  is small assume that the Zener does not conduct implies  $I_Z=0$

$$I_R = I_L = \frac{20}{200+180} = 52.6mA$$

$V_S = V_L = 20 - 200 \cdot I_R = 20 - 200 \cdot 52.6m = 9.48V < 10V \therefore$  assumption that  $I_Z$  is zero is correct.

b)  $R_L=450\Omega$  implies Zener conducts so  $V_L=V_Z=10V$  as per the given data

$$I_L = \frac{10}{450} = 22.2mA$$

$$I_R = \frac{20-10}{200} = 50mA$$

$$I_Z = I_R - I_L = 30mA - 22.2mA = 7.8mA$$

$$P_Z = I_Z \cdot V_Z = 7.8 \cdot 10 = 78mW < 350mW$$

c) When zener draws max power,

$$I_Z = \frac{P_Z}{V_Z} = \frac{350}{10}mA = 35mA$$

$$I_R = \frac{20-10}{200} = 50mA$$

$$I_L = I_Z - I_R = 15mA$$

$$R_L = \frac{V_R = V_L}{I_L} = \frac{10}{50m} = 200\Omega$$

## 2 Determine the range of $V_i$ in which the zener operates

For  $V_Z=20V$ ,  $P_{Z_{\max}}=1200mW$ ,


- When the zener just starts conducting,  $I_Z=0$

$$V_Z=20V; I_R=I_L=\frac{20}{1.25}=16mA$$

$$V_i = V_Z + I_R \cdot 220 = 20 + 16m \cdot 220 = 23.52V$$

- When the zener current is max  $I_Z = I_{Z_{\max}}$
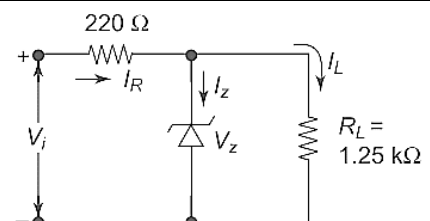
$$I_{Z_{\max}} = \frac{P_{Z_{\max}}}{V_Z} = \frac{1200}{20} = 60mA \quad I_L = 16mA$$



$$I_R = I_L + I_{Z_{max}} = 16 + 60 = 76 \text{mA}$$

$$V_i = V_Z + I_R * 220 = 20 + 76 \text{m} * 220 = 36.72 \text{V}$$

Hence observed that for  $V_i$  ranging from 23.52 V to 36.72V  $V_L$  shall remain constant at 20V

### 3. Design a Zener diode voltage regulator to meet the following requirements

Unregulated DC input voltage,  $V_i = 13 - 17 \text{V}$

Load current,  $I_L = 10 \text{mA}$

Regulated output voltage,  $V_o = 10 \text{V}$

Minimum zener current,  $I_{Z_{min}} = 5 \text{mA}$

Maximum power dissipation in zener,  $P_{D_{max}} = 500 \text{mW}$

Maximum power dissipation is  $P_{D_{max}} = P_D = I_{L_{max}} V_Z$

$$I_{Z_{max}} = \frac{P_D}{V_Z} = \frac{500 \text{m}}{10} = 50 \text{mA}$$

Maximum current through the zener diode is  $\frac{V_{i_{max}} - V_o}{R} - I_{L_{min}} < I_{Z_{max}}$

$$\frac{17 - 10}{R} - 0 < 50 \text{mA}$$

$$R > \frac{7}{50 \text{m}}$$

$$R = 140 \Omega$$

Minimum current through the zener diode is

$$\frac{V_{i_{min}} - V_o}{R} - I_{L_{max}} > I_{Z_{min}}$$

$$\frac{13 - 10}{R} - 10 \text{mA} > 5 \text{mA}$$

$$R < \frac{3}{15 \text{mA}}$$

$$R = 200 \Omega$$

Combining above we can write

$$140 \Omega < R < 200 \Omega$$

$$R = \frac{140 + 200}{2} = 170 \Omega$$

$$R_L = \frac{V_o}{I_L} = \frac{10}{10 \text{mA}} = 1 \text{k}\Omega$$

### 4. A 24V, 600mW Zener diode is used for providing a 24V stabilized supply to a variable load. If the input voltage is 32V, calculate

i. The value of series resistance required

ii. Diode current when the load is  $1200 \Omega$

Since no variation in input,  $V_{i_{max}} = V_{i_{min}} = V_i = 32 \text{V}$

$$I_{Z_{max}} = \frac{P_D}{V_Z} = \frac{600 \text{m}}{24} = 25 \text{mA}$$

$$\frac{V_{i_{max}} - V_o}{R} - I_{L_{min}} < I_{Z_{max}}$$



But  $I_{L_{\min}} = 0$  hence  $\frac{32-24}{R} - 0 < 25m$

$$R > \frac{8}{25m} \quad \text{implies } R = 320\Omega$$

$$I_L = \frac{V_o}{R_L} = \frac{24}{1200} = 20mA$$

Diode current is given by

$$I_Z = \frac{V_i - V_o}{R} - I_L$$

$$I_Z = \frac{32 - 24}{320} - 20m$$

$$I_Z = 5mA$$

5. A 9V reference source is to be designed using a zener diode and a resistor connected in series to a 30V supply. Select suitable components and calculate the circuit current when the supply drops to 27V. Take  $I_{ZT} = 20mA$

Since load current is not given it is unloaded voltage regulator.  $I_{ZT}$  is the test current which lies between  $I_{L_{\min}}$  and  $I_{Z_{\max}}$   $V_o = V_Z = 9V$

$$I = I_Z = \frac{V_i - V_o}{R}$$

$$R = \frac{V_i - V_o}{I_{ZT}} = \frac{30 - 9}{20m} = 1.05k\Omega$$

When  $V_i = 27V$

$$I_Z = \frac{V_i - V_o}{R} = \frac{27 - 9}{1.05k} = 17.14mA$$

#### LINKS TO PROBLEMS:

PROBLEM: ZENER DIODE REGULATOR (2):

<https://www.youtube.com/watch?v=LtWMuoQKMic>

PROBLEM: ZENER DIODE REGULATOR (3):

<https://www.youtube.com/watch?v=HBaddgGeIrM>

PROBLEM: ZENER DIODE REGULATOR (4):

<https://www.youtube.com/watch?v=Glio3MxT2Q>

PROBLEMS: ZENER DIODE (PART 1): <https://www.youtube.com/watch?v=rE4wC7h8uWo>

PROBLEMS: ZENER DIODE (PART 2): <https://www.youtube.com/watch?v=dKw6lBy8Xzc>

## Photodiode

- It is a semiconductor device that **converts light into an electrical current**.



Fig.1.31: Photodiode

- A photodiode is a **PN junction (silicon / germanium)** operates in **reverse bias region** as shown in Fig.1.32.

- When a light is made **to illuminate the PN junction, covalent bonds are ionized**. This generates hole and electron pairs.
- **Photocurrents are produced** due to generation of electron-hole pairs that are formed **when photons of energy more than 1.1eV hits the diode**.
- When the photon enters the depletion region of diode, it hits the atom with high energy. This results in release of electron from atom structure. After the electron release, free electrons and hole are produced.
- Due to the electric field, electron hole pairs moves away from the junction. Hence, **holes move to anode and electrons move to cathode to produce photo current**.
- The **photon absorption intensity and photon energy are directly proportional to each other**. When energy of photon is less, the absorption will be more.

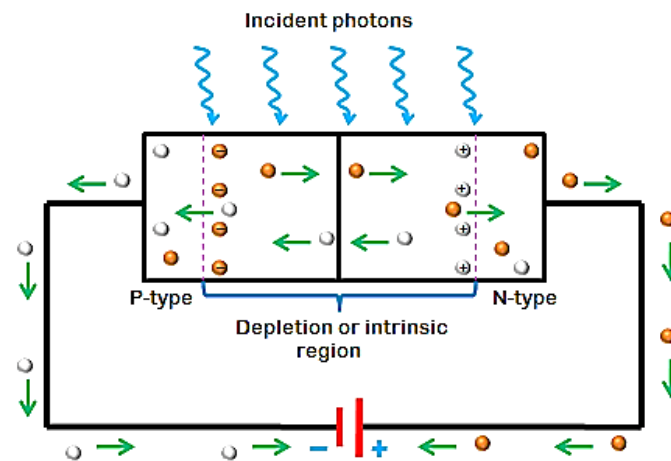


Fig.1.32: Photodiode under reverse bias

LINKS TO VIDEOS: Photodiode What, How it Works Explained: <https://www.youtube.com/watch?v=kry1aGCU2Go>

## Light Emitting Diode (LED)

1. Light-emitting diode (LED) is a two terminal p-n junction semiconductor diode which emits light when activated.
2. When a **suitable current is applied to the terminals**, electrons are able to **recombine with electron holes** within the device, **releasing energy** in the form of photons. This effect is called **electroluminescence**.
3. The process of light emission in pn junctions is illustrated in Fig.1.33.
4. **The metal contact of p material is made much small** to permit the emergence of maximum number of photons so that in an LED, **the light lumens generated per watt of electric power is high**. Intensity of light increases almost linearly with **forward current**, depending on the material used.

- The voltage levels of LEDs are **1.7V to 3.3V** which is compatible with solid state circuits. The response time is short and light contrast is good. **LEDs emit red, green, orange or blue.**
- LEDs are used in several display applications, such as 8 segment display of numbers 0 to 9, LED TVs.

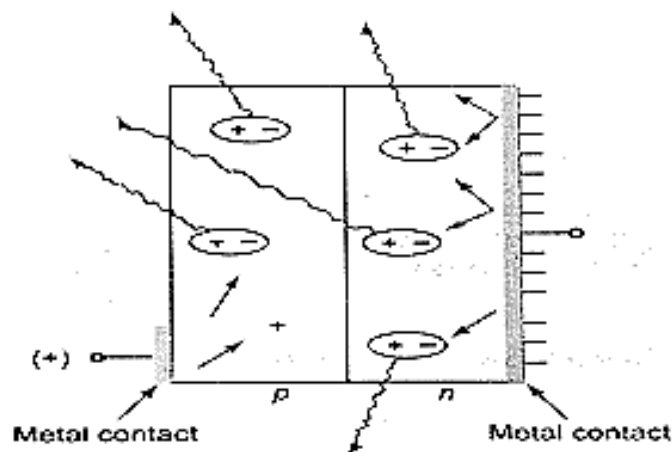


Fig.1.33: Light emission in PN junction

**LED - Working, Advantages and Types:** <https://www.youtube.com/watch?v=kaKLmKhUrf4>

### Photo Coupler

- Photo coupler is a package of an LED and photodiode where circuits are electrically isolated** as shown in Fig.1.34.
- The LED is forward biased and the photodiode is reverse biased.** The output is available across  $R_2$

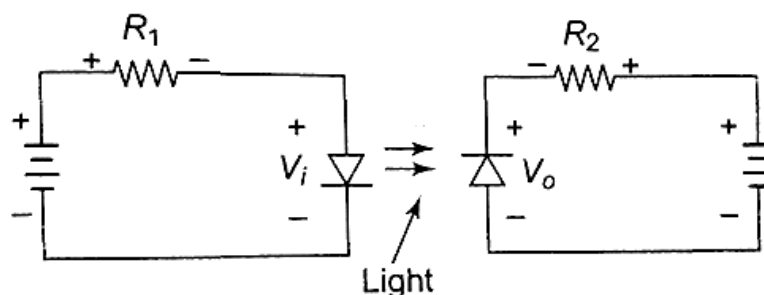


Fig.1.34: Photo coupler

- The **output signal of one circuit can be controlled by varying input signal in another circuit**, where the two circuits are **ELECTRICALLY ISOLATED**.
- A powerful light emitting diode (LED) is connected across a variable voltage source. By adjusting the input voltage  $V_i$  across the LED, the intensity of the light emitted from the LED can be controlled. The variable source and the LED form the input circuit of the photocoupler.
- A photodiode is present in front of the LED so that the light from the LED directly strikes the junction of the photodiode. The photodiode is in reverse biased

condition. The reverse biased circuit of the photodiode forms the output circuit of the system.

6. Initially, no voltage is applied to the LED; hence the LED does not glow. In this condition there would be only **dark current** flowing through the output circuit. Dark current is the reverse saturation current of the reverse biased photodiode when it is entirely dark.
7. If the voltage across the LED increased, the LED starts glowing and at the same time intensity of the light increases with increasing input voltage across the LED. With increasing light intensity, the reverse current in the photodiode increases, since the reverse current in a photodiode is linearly proportional to the intensity of light falling on the photodiode junction. Also, if the **intensity of light in the input is decreased, the output photodiode current will also decrease.**
8. The key advantage of the photocoupler is the **isolation between two circuits.**

### LM 78XX series Voltage Regulator

1. LM78XX is a family of **self-contained fixed linear voltage regulator integrated circuits** commonly used in electronic circuits requiring a regulated power supply due to their ease-of-use and low cost.
2. For ICs within the 78XX family, the XX is replaced with two digits (XX = 05, 06, 08, 10, 12, 15, 18 or 24), indicating the output voltage (for example, the 7805 has a 5-volt output, while the 7812 produces 12 volts).
3. They are +ve voltage regulators; they produce a voltage that is +ve relative to a common ground.
4. LM78XX ICs have three terminals and support an input voltage anywhere from around 2.5 volts over the intended output voltage up to a maximum of 35 to 40 volts depending on the model, and typically provide 1 or 1.5 amperes of current.

### 7805 Fixed IC Voltage Regulator

5. This fixed linear voltage regulator has **Pin 1 - input, Pin 2 - output and Pin 3 - connected ground.** The LM7805 has an output voltage of **+5V** and a maximum load current **over 1 A.**

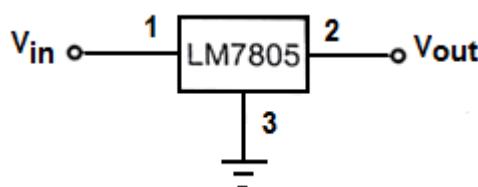


Fig.1.35: 7805 Fixed IC Voltage Regulator

**PIN 1: Input**


This pin is used to apply the input voltage which can be in the range of **7V to 35V**.

**PIN 2: Ground**

This pin is connected to ground.

**PIN 3: Output**

6. This pin is used to take the regulated output. It will be 5V
7. The output of the rectifier is an unregulated DC Voltage, therefore two capacitors are required to obtain a regulated DC voltage and are connected as shown in the Fig.1.36.

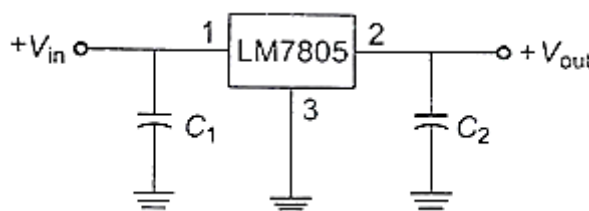

**Fig.1.36: LM7805 with capacitor**


8. Capacitor  $C_2$  at the output side is used to avoid transient changes in the voltages due to changes in load and a Capacitor  $C_1$  at the input side of regulator is used to avoid ripples if the filtering is far away from regulator.

**78XX Voltage Regulator:** <https://www.youtube.com/watch?v=rPb0p7N1O00>


**Question Bank**

1. Explain the operation of pn junction diode under forward and reverse bias condition
2. List the diode parameters required for the construction of diode characteristics
3. Define the following terms
  - a. Dynamic resistance
  - b. Rev, saturation current
  - c. Rev. breakdown voltage
4. Explain the characteristics of an ideal diode
5. Explain the piecewise-linear characteristics of a diode
6. Draw the DC equivalent circuit of a diode and explain
7. Explain the operation of zener diode along with its characteristics
8. Define rectifier? What are the different types of rectifiers?
9. With circuit diagram explain the operation of half wave rectifier. Draw the input and output waveforms.
10. With circuit diagram explain the operation of center tapped full wave rectifier. Draw the input and output waveforms.
11. With circuit diagram explain the operation of full wave bridge rectifier. Draw the input and output waveforms.
12. Explain the operation of half wave rectifier with capacitor filter.
13. Explain the operation of full wave rectifier with capacitor filter.
14. Explain the operation of full wave bridge rectifier with capacitor filter.
15. Explain how zener diode can be used as voltage regulator

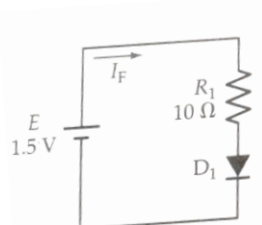
16. Explain the operation of 7805 fixed IC voltage regulator.
17. Write a short note on (i) Light emitting diode (ii) Photo coupler (iii) Photo diode
18. Plot the forward and reverse characteristics of a diode for the following data
  - a. Forward voltage drop = 0.6V
  - b. Reverse breakdown voltage = 100V
  - c. Reverse saturation current =  $1\mu\text{A}$
  - d. Forward current = 100mA at a forward voltage of 0.65V
  - e. Forward current = 250mA at a forward voltage of 0.7V
19. Determine the dynamic resistance at a forward current of 20mA for the diode characteristics given in the Fig.1.6
20. Construct a piecewise linear characteristics for a silicon diode which has a  $0.2\Omega$  dynamic resistance and a 200mA maximum forward current.
21. Calculate  $I_F$  for the diode in the given circuit assuming that  $V_F = 0.7\text{V}$  and  $r_d = 0$ . What is the current if we consider  $r_d = 0.2\Omega$



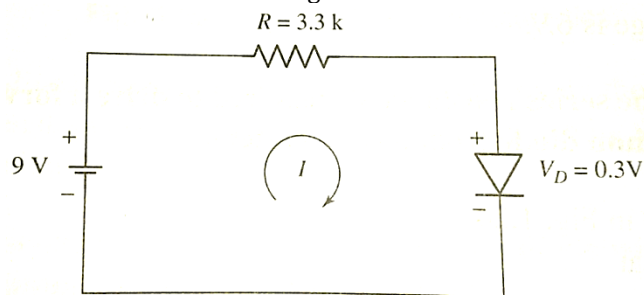22. Calculate the diode current for the circuits given below



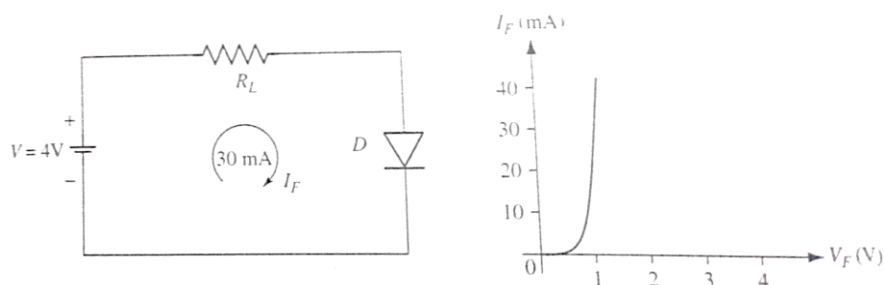23. Using the device characteristics in the Figure below, determine the required load resistance for the circuit given in the Figure to give  $I_F = 30\text{mA}$



24. A sinusoidal voltage of peak value 40V and frequency 50Hz is applied to a half wave rectifier having a load resistor of  $800\Omega$  and  $R_f$  of the diode is  $8\Omega$ . Calculate
  - a. Peak, DC and RMS value of load current
  - b. DC output power
  - c. AC input power
  - d. rectifier efficiency
25. The input to a half wave rectifier is given through a 2:1 transformer from a supply of 240V, 50Hz. If  $R_f = 0$  and  $R_L = 500\Omega$  determine
  - a. DC load voltage
  - b. RMS load voltage
  - c. PIV
  - d. rectifier efficiency
  - e. DC power delivered to load
  - f. freq of output waveform

26. A sinusoidal voltage of peak value 40V and frequency 50Hz is applied to a full wave rectifier having a load resistor of  $800\Omega$  and  $R_f$  of the diode is  $8\Omega$ . Calculate
- Peak, DC and RMS value of load current
  - DC output power
  - AC input power
  - rectifier efficiency
27. The input to a full wave rectifier is given through a 10:1 transformer from a supply of  $230\sin 314t$ . If  $R_f = 50\Omega$  and  $R_L = 500\Omega$  determine
- DC load voltage
  - RMS load voltage
  - PIV
  - rectifier efficiency
  - DC power delivered to load
  - freq of output waveform
28. A sinusoidal voltage of peak value 40V and frequency 50Hz is applied to a full wave bridge rectifier having a load resistor of  $800\Omega$  and  $R_f$  of the diode is  $8\Omega$ . Calculate
- Peak, DC and RMS value of load current
  - DC output power
  - AC input power
  - rectifier efficiency
29. The input to a full wave bridge rectifier is given through a 10:1 transformer from a supply of  $230\sin 314t$ . If  $R_f = 50\Omega$  and  $R_L = 500\Omega$  determine
- DC load voltage
  - RMS load voltage
  - PIV
  - rectifier efficiency
  - DC power delivered to load
  - freq of output waveform
30. Design a Zener diode voltage regulator to meet the following requirements
- DC input voltage,  $V_i = 20V$
  - Load current,  $I_L = 20mA$
  - DC output voltage,  $V_o = 10V$
  - Minimum zener current,  $I_{Z_{min}} = 10mA$
  - Maximum zener current,  $I_{Z_{max}} = 100mA$
31. Design a Zener diode voltage regulator to meet the following requirements
- DC input voltage,  $V_i = 10V \pm 2V$
  - Load current,  $I_L = 10mA$
  - DC output voltage,  $V_o = 5V$
  - Minimum zener current,  $I_{Z_{min}} = 5mA$
  - Maximum power dissipation,  $P_{Z_{max}} = 400mW$

# Problems on rectifiers

**Q1.** The applied input a.c. power to a half-wave rectifier is 100 watts. The d.c. output power obtained is 40 watts. (i) What is the rectification efficiency ?


**Q2.** An a.c. supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10 : 1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal

**Q3.** A crystal diode having internal resistance  $r_f = 20\Omega$  is used for half-wave rectification. If the applied voltage  $v = 50 \sin \omega t$  and load resistance  $R_L = 800\Omega$ , find : (i)  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$  (ii) a.c. power input and d.c. power output (iii) d.c. output voltage (iv) efficiency of rectification.


**Q4.** A half-wave rectifier is used to supply 50V d.c. to a resistive load of  $800\Omega$ . The diode has a resistance of  $25\Omega$ . Calculate a.c. voltage required.

**Q5.** A full-wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at  $20\Omega$ . The transformer r.m.s. secondary voltage from centre tap to each end of secondary is 50 V and load resistance is  $980\Omega$ . Find : (i) the mean load current (ii) the r.m.s. value of load current.

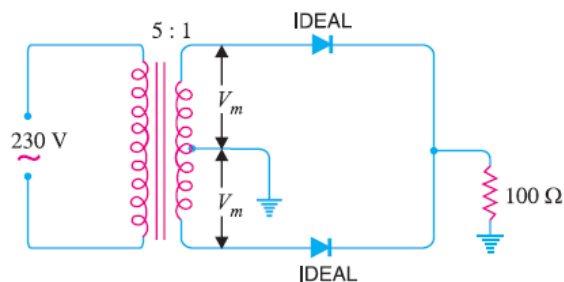**Q6.** In the centre-tap circuit shown , the diodes are assumed to be ideal i.e. having zero internal resistance. Find :(i) d.c. output voltage(ii) peak inverse voltage (iii) rectification efficiency.




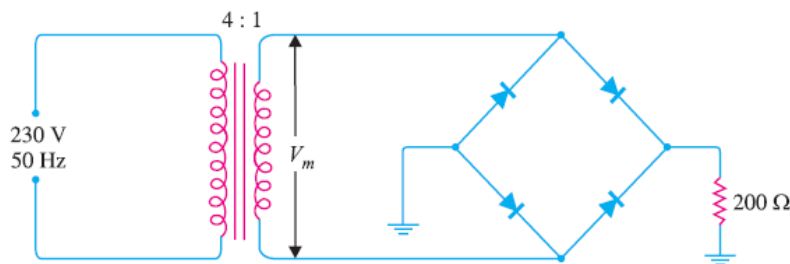**Q7.** In the bridge type circuit shown , the diodes are assumed to be ideal. Find : (i) d.c. output voltage (ii) peak inverse voltage (iii) output frequency. Assume primary to secondary turns to be 4.






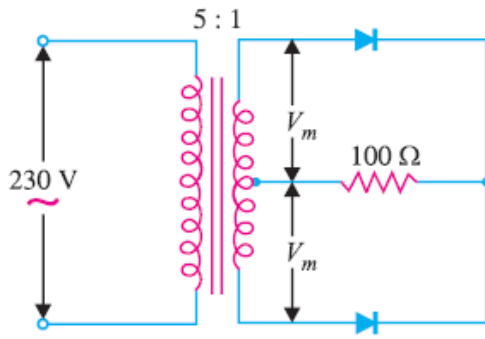**Q8.** Show the centre-tap and bridge type circuits having the same load resistance and transformer turn ratio. The primary of each is connected to 230V, 50 Hz supply. (i) Find the d.c. voltage in each case. (ii) PIV for each case for the same d.c. output. Assume the diodes to be ideal.




(i)

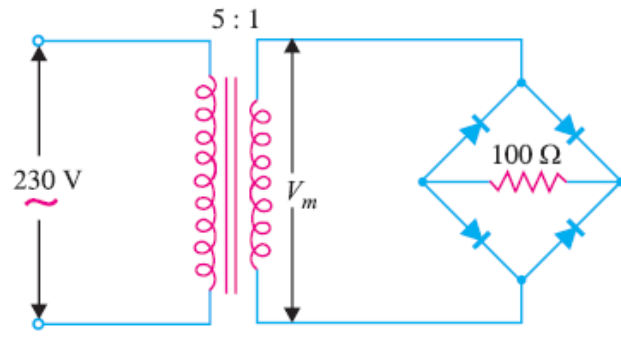

(ii)

**Q9.** The four diodes used in a bridge rectifier circuit have forward resistances which may be considered constant at  $1\Omega$  and infinite reverse resistance. The alternating supply voltage is 240 V r.m.s. and load resistance is  $480\Omega$ . Calculate (i) mean load current and (ii) power dissipated in each diode.

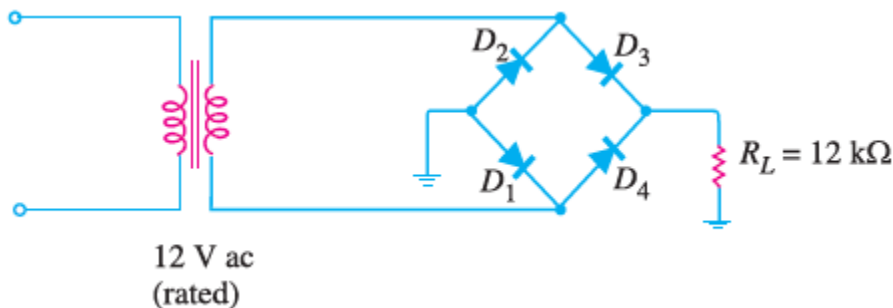**Q10.** The bridge rectifier shown uses silicon diodes. Find (i) d.c. output voltage (ii) d.c. output current. Use simplified model for the diodes



**Q11.** A power supply A delivers 10 V dc with a ripple of 0.5 V r.m.s. while the power supply B delivers 25 V dc with a ripple of 1 mV r.m.s. Which is better power supply ?

**Q12.** For the circuit shown, find the output d.c. voltage

